

MARCH
1956

● EXPERIMENTS WITH 144 Mc. UNDERGROUND ● BAND-
SPREADING THE SUPER-PRO ● QRP T/R ANTENNAE SWITCHING
FOR 144 AND 288 Mc. ● MOBILE TRANSMITTER AND ANTENNA

Amateur Radio

AMATEURS AND TECHNICIANS!

This is the **BEST SPOT** in Melbourne for . . .

RADIO PARTS AND ACCESSORIES!

Distributors of **ADVANCE, PALEC, TAYLOR**, and
UNIVERSITY Meters and Test Equipment.

And such well-known Radio
Accessories as . . .

- AEGIS products
- TRIMAX products
- A & R products
- FERGUSON products
- ROLA products
- JENSON products
- I.R.C. products
- ALPHA products
- CYLDON products
- B.S.R. products
- MORGANITE Potentiometers
- STENTORIAN Speakers
- STEANE'S Amplifiers
- SUPERSPEED SOLDERS
- GOLDRING products
- CONNOISSEUR products
- EDDYSTONE products
- M.S.P. products
- BELLING-LEE products
- DUCON products
- SIMPLEX products
- BULGIN products
- OAK products
- LEAK Amplifiers
- QUAD Amplifiers
- RADJOTRON Valves
- PHILIPS Valves
- BRIMAR Valves
- MONARCH Gramo. Motors
- GARRARD Gramo. Motors
- COLLARO Motors, Pickups



1/-



208 LT. LONSDALE ST., MELB.

PHONE: FB 3731 — OPEN SATURDAY MORNINGS!

"HAM" RADIO SUPPLIERS

(KEN MILLBOURN, PROP.)

Bargains Galore - - Compare These Reduced Prices

NOTE THESE VALVE PRICES

Look at these Bargain				Priced NEW VALVES—			
1A5	2/6	6K8	15/-	128J7	10/-	U10	2/6
1B5	2/6	6L7	10/-	128K7	10/-	VR18	2/6
1H5	10/-	6L7G	7/6	128Q7	2/6	VR19	2/6
1K4	5/-	6N7	10/-	128Q7GT	2/6	VR21	2/6
1K5	10/-	6N8	15/-	25AC5	10/-	VR22	2/6
2A3	10/-	6Q7G	5/-	807	20/-	VR32	2/6
2A5	10/-	6R7G	10/-	816	15/-	VR35	2/6
3Q5	5/-	6SC7	10/-	834	£1	VR38	2/6
5V4	10/-	6SF7	12/6	866	£1	VR66	2/6
6AG7	15/-	6SJ7GT	12/6	884	£1	VR75	15/-
6B8	15/-	6SK7GT	12/6	954	10/-	VR102	5/-
6C8	7/6	6SS7	12/6	955	10/-	VR103	5/-
6E5	10/-	7A6	5/-	957	10/-	VR105	15/-
6F5	7/6	7B8	5/-	1625	£1	VR150	15/-
6F6	10/-	7C7	2/6	5763	25/-	VT30	2/6
6K6	7/6	7E6	5/-	EF50	10/-	VT51	2/6
6K7G	7/6	7W7	5/-	RK34	7/6	VT52	10/-

Full stocks of new Valves available. Prices on request.

VR90 Voltage			Regulator, 15/-.				
Following list are ex			Disposals, guaranteed—				
1K5	5/-	5U4	12/6	6H6	5/-	12A6	10/-
1K7	5/-	6AC7	10/-	6SJ7G	10/-	12K8	10/-
1L4	5/-	6AG5	10/-	6SK7G	10/-	1625	15/-
1S5	10/-	6C5	10/-	6SL7	15/-	CV92	15/-
2X2	10/-	6C8	5/-	6SN7	7/6	EF50	5/-
3A4	5/-	6D6	5/-				

Step-down Transformers, 230v. to 80v.-90v.-100v. at 2.5 amp.
Brand new £2/10/-

THIS MONTH'S SPECIAL NEW ENGLISH VT127 — 4/11 (4 VOLT 807) Octal Base.

Filament Transformers, 2.5v. 16 amp. e.t. for 866s, etc., also 65v. at 150 Ma. 6.3v. 1 amp., band new £2
Filament Transformers, 10v. 3 amp., 12.6v. 2 amp., 6.3v. at 300 Ma., brand new £2
Filament Transformers, 6.3v. 4 amp., 6.7 v. 4 amp., 6.7v. 4 amp., brand new £2
Filament Transformer—Prim.: 240v.; Sec.: Three windings of 6.3v. at 2 amp., one 5v. at 4 amp. Few only £2
Filament Transformer—Prim.: 240v.; Sec.: 13 taps between 17 and 35 volts £2
2.5v. or 4v. Filament Transformers 15/- each
Bendix RA1B Power Supplies, 240 volt AC, 24v. at 1 amp. output 230v. HT £5 each
Genemotor Power Supply, SCR522, 24v. input, 150v. and 300v. output at 300 Ma. Includes relay, voltage regulator, etc. A gift at £1. Too heavy for postage.
Chokes, 15 Henry, 100 Ma. 10/- each
Chokes, 15 Henry 175 Ma. 20/- each
2 uF, 1000v. block type Chanex Condensers 12/6

AT5 Transmitters, less valves and dust covers £3
AT5 Aerial Coupling Units, complete with meter, £1/10/-
AR5 Receivers, complete with valves, 150 Kc. to 20 Mc., £15
RAX Receivers, complete with valves, 150-1500 Kc., £16/10/-
Amer. Loran Receivers, contains 26 valves, 1 100 Kc. xial, £15
BC733D Crystal Locked Receiver, 10 valves, 100-120 Mc., £3
SCR522 American Transceiver. Frequency: 100 to 150 Mc. In clean condition, less valves £10
CRO Indicators, complete with 6BP1 CRO tube, six EF36s, one VR54, one 2X2 valve. Brand new, to clear £7/10/-
Power Transformers, 40 Ma., 250-0-250, 6.3v. 3 amp., new, 15/-
Filter, FL8, American. Just arrived. Brand new 25/-
Class C Wavemeter, Aus. A.W.A., less vibrator supply, £8/10/-
AWE1 Wavemeter, Aust. high freq., 145 to 165 Mc., £5/17/6
Filament Transformer, 10v. 3 amp., 5v. 2 amp., brand new, 30/-
Transformers, high amp., low voltage. Input volts 230, output volts 13-15-14-15, at sixty amps. £5
American Murdoch Headphones, 2,000 ohms DC resistance, complete with extension plug 25/- pair
Inter-Com. Units, English. Contains two valves, transformers, P.M.G. key switch, resistors, etc. To clear 12/6 each
Shielded Cable with two 12-pin Plugs 7/6
Seven-core Cable, not shielded 8d. yard
Co-ax Connectors, Ampenol type, male and female 7/6 pair
Co-ax, indoor type, cotton covered 1/- yard
Co-ax Cable, any length, 50 ohms 1/9 yard
Lockal Sockets 1/6 each
Valve Sockets, ceramic, 8-pin Octal 2/6
Valve Sockets, ceramic, 5-pin 5/-
Relays, A.W.A. Aerial Change-over type, 12v. 15/-
English Carbon Mike Transformers, new 5/-

LARGE STOCK OF CRYSTALS

100 Kc. R.C.A. Crystals £4
1000 Kc. Crystals, DC11 holder, with two pig-tail connect., 35/-
3.5 Mc. Marker Crystals, latest miniature type complete with socket £2/10/-
Gold Plated Marker and Commercial Crystals, price on request.
Delivery in seven days.

Following is a list of Crystal Frequencies available for immediate delivery. £2 each—

2081.2 Kc.	3592.5 Kc.	7028 Kc.	7100 Kc.	8011 Kc.
2103.1 Kc.	6350 Kc.	7028.5 Kc.	7106.7 Kc.	8155.714 Kc.
2112.5 Kc.	6375 Kc.	7032 Kc.	7110 Kc.	8161.538 Kc.
2208.1 Kc.	6450 Kc.	7032.6 Kc.	7120 Kc.	8171.25 Kc.
2218.7 Kc.	6550 Kc.	7035 Kc.	7121 Kc.	8176.923 Kc.
3282.5 Kc.	7004 Kc.	7040 Kc.	7125 Kc.	8182.5 Kc.
3300 Kc.	7005 Kc.	7042.65 Kc.	7126 Kc.	8183.5 Kc.
3335 Kc.	7010 Kc.	7045 Kc.	7130 Kc.	8137.2 Kc.
3600 Kc.	7010.7 Kc.	7047 Kc.	7134 Kc.	8320 Kc.
3625 Kc.	7011.5 Kc.	7050 Kc.	7140 Kc.	10.511 Mc.
4285 Kc.	7011.75 Kc.	7053.5 Kc.	7145 Kc.	10.515 Mc.
4495 Kc.	7012 Kc.	7063 Kc.	7150 Kc.	10.524 Mc.
5050 Kc.	7016 Kc.	7064 Kc.	7156 Kc.	10.530 Mc.
5300 Kc.	7018 Kc.	7068 Kc.	7162.5 Kc.	10.5465 Mc.
5360 Kc.	7021 Kc.	7072 Kc.	7163 Kc.	10.556 Mc.
5456 Kc.	7021.5 Kc.	7073.5 Kc.	7174 Kc.	12.863 Mc.
5530 Kc.	7021.715 Kc.	7075 Kc.	7175 Kc.	12.915 Mc.
5700 Kc.	7024 Kc.	7077 Kc.	7205 Kc.	14.322 Mc.
3750 Kc.	7025 Kc.	7080 Kc.	8009 Kc.	

5A MELVILLE STREET, HAWTHORN, VICTORIA

North Balwyn Tram Passes Corner, near Vogue Theatre.

Phone: WA 6465

Money Orders and Postal Notes payable North Hawthorn P.O. Packing Charge on all goods over 10 lbs. in weight, 5/- extra.

EDITOR:

T. D. HOGAN, VK3HX.

MANAGING EDITOR:

J. G. MARS LAND, VK3NY.

TECHNICAL EDITOR:

K. E. PINCOTT, VK3AFJ.

TECHNICAL STAFF:

J. C. DUNCAN, VK3VZ.

D. A. NORMAN, VK3UC.

R. S. FISHER, VK3OM.

A. E. MORRISON, VK4MA.

COMPILATION:

R. W. HIGGINBOTHAM, VK3RN.

CIRCULATION:

I. K. SEWELL, VK3IK.

ADVERTISING REPRESENTATIVE:

BEATRICE TOUZEAU,
96 Collins St., Melbourne, C.I.
Telephone: MF 4505

PRINTERS:

"RICHMOND CHRONICLE,"
Shakespeare St., Richmond, E.I.
Telephone: JB 2419.

MSS. and Magazine Correspondence should be forwarded to the Editor, "Amateur Radio," C.O.R. House, 191 Queen Street, Melbourne, C.I. on or before the 8th of each month.

Subscription rate in Australia is 12/- per annum, in advance (post paid) and A15/- in all other countries.

Wireless Institute of Australia (Victorian Division) Rooms' Phone Number is MY 1087.

WI BROADCASTS

All Amateurs are urged to keep these frequencies clear during, and for a period of 15 minutes after, the official broadcasts.

VK3WI: Sundays, 1100 hours EST, 7146 Kc. and 2000 hours EST 50 and 144 Mc. No frequency checks available from VK3WI. Intra-state working frequency, 7125 Kc.

VK3WI: Sundays, 1130 hours EST, simultaneously on 3573 and 7146 Kc., 51.016 and 146.25 Mc. Intra-state working frequency 7135 Kc. Individual frequency checks of Amateur Stations given when VK3WI is on the air.

VK4WI: Sundays, 0900 hours EST, simultaneously on 3580 and 14943 Kc., 3580 Kc. channel is used from 0915 hours to 1015 hours each Sunday for the W.I.A. Country hook-up. No frequency checks available.

VK3WI: Sundays, 1200 hours SAST, on 7146 Kc. Frequency checks are given by VK3MD and VK3WI by arrangements on all bands to 50 Mc.

VK3WI: Sundays, 1930 hours WAST, on 7146 Kc. No frequency checks available.

VK3WI: Sundays, at 1000 hours EST, on 7146 Kc. and 146.5 Mc. No frequency checks are available.

VK3WI: Sundays, 1000 hours EST, simultaneously on 3.5, 7, 14 and 144 Mc. Individual frequency checks of Amateur Stations given when VK3WI is on the air.

Published by the Wireless Institute of Australia,
C.O.R. House, 191 Queen Street,
Melbourne, C.I.

EDITORIAL



FEDERAL CONVENTIONS

When a man's stomach is full and his appetite is satisfied, like other animals, he is usually content to drowse and ignore the world in general. On the other hand when the gnawing pangs of hunger bite at his vitals, he becomes ferocious and vociferous.

Judging by the growing clamour for more privileges and the removal of licence restrictions, members of the Institute are awakening from the lethargy which has been apparent since 1953. There is a general awareness of the necessity for united action on the part of Divisions.

How can united action be best achieved?

The answer is obvious. "Federal Council must meet and thrash out a course of action."

In 1953 at the Twenty-third Convention it was decided that owing to increased costs and the lack of contentious items—following intensive and successful post-war campaign—Annual Conventions were an unnecessary financial drain on the Divisions. Council therefore resolved that the next Convention would not be held until business of sufficient importance to warrant the expense arose. In the meantime, Divisions

were morally bound to create a fund and set aside a reasonable amount each year in readiness for this event whenever it occurred.

Since 1953 a new Division—VK9 (Papua and New Guinea)—has been formed. Problems have arisen concerning: Constitution, Contests, Band Allocation, Mobile, Novice and TV Licenses. Hence it now appears that Council must meet as soon as possible.

While much of the business of the Institute can be, and is, conducted by mail, there is no known substitute for personal contact and round table conferences when matters affecting high policy are involved. Furthermore, such personal contact is essential to maintain proper liaison between Divisions and avert the calamitous drift from "Federation."

"United we stand—divided we fall."

How can YOU expect Federal Executive to carry out your wishes unless you issue instructions through your Federal Councillor.

Keep yourself informed of Federal affairs, demand action now through the right channels. Don't waste energy on individual campaigns, boost and use the Institute's strength to the full.

FEDERAL EXECUTIVE.

THE CONTENTS

Experiments with 144 Mc. Under-ground	2	QRP T/R Switching for 144 and 288 Mc. Antennae	12
Transformer Theory and Practice, Part Two	5	A Mobile Transmitter and Antenna	14
Bandspredding the Super-Pro on all Bands	9	DX Activity by VK3AHH	17
Eighth Annual Uruga Convention	10	Prediction Chart for March, '56	18
Book Review—"Introduction to T.V. Servicing"	10	Short Wave Listeners' Section	18
Further Notes on the Transmitter with Low Harmonic Output	11	Fifty-six Megacycles and Above	19
		Federal, QSL, and Divisional Notes	20

Experiments with 144 Mc. Underground

BY P. J. HEALY,* VK2APQ

ON Sunday, 4th December, 1955, a party consisting of members of V.h.f. Group of the N.S.W. Division of the Wireless Institute of Australia and the Sydney University Speleological Society, carried out some very interesting experiments on 144 Mc. in the Jenolan Caves area of N.S.W.

The aim was to ascertain if communication was possible between different sections of the caves using 144 Mc. Walkie-Talkie equipment. It was with some doubt as to what measure of success would be achieved, that the trip to Jenolan Caves was made by Perc. Healy, VK2APQ; Ted Howard, VK2XX; Charlie Fryer, VK2NP; Horrie Lapthorn, VK2HL; Vic Cole, VK2VL; John Thornthwaite, VK2ATO; Bob Ridgley, VK2ZAR; Cec. Cronan, Darrell Price, Wal Jacobs, who were joined at Jenolan by Brian O'Brien, Cres. Wallace, Laurie Bishop, Adrian Hunt, Tom Draper, and John Lehane, of the Sydney University Speleological Society, but the results achieved were beyond all expectations as the following details will indicate.

The equipment used consisted of four walkie-talkie units, including one crystal-controlled and three modulated oscillators, all with super-regenerative receivers, each with an input to the final stage of approx. 0.4 watt. The mobile units were two crystal-controlled transmitters running 6 watts input, receivers, a super-regen. superhet, and a Goon set. Antennae were quarter wave whips on the walkie-talkies, a three element beam and a galloway on the mobile unit.

The first experiment was carried out in the Glass Cave, which is not open to the public. This cave is located about half a mile direct air line to the north of the Caves House, "accessible" by track requiring a two-mile trip over the ridge and down a 700 foot drop with numerous hairpin bends.

PLAN OF AREA

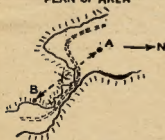


Fig. 1

Entrance into the Glass Cave is made through a very narrow opening located 150 feet above the valley floor, necessitating a climb up a steep slope of approx. 35 degrees from horizontal, to the base of a limestone outcrop.

Fig. 1 gives an indication of the position of the cars operating as base station "A" located on the river flat in

the floor of the valley to the cave mouth "B", a distance in a direct line of approx. one-third of a mile. The track from the car to cave was through a gorge along the river bed, then the 150 foot ascent.

Fig. 2 is a scale plan of the interior of this cave, and indicates the relative positions of "C" "D" "E" and "F" from which tests were made.

Three parties, equipped with walkie-talkies, entered the cave and operated from positions "C" "D" and "E". The plan was to endeavour to relay information back to "A" via the fourth walkie-talkie located at "B".



An interior view of Cavern "C" in the Glass Cave. The ladder descends down 25 feet. Refer Fig. 2.

It will be noted from Fig. 2 that the entrance to the cavern "C", which is 50 feet high, is made through a very narrow chimney and a drop of 25 feet to the floor. While to "D" required a 20 foot climb through a narrow neck to a chamber 15 feet high, and to "E" through a "Flattener" about one foot high to a chamber 15 feet high.

The first test made was between "B" and "C", the path between "A" and "B" had been previously checked by all parties. Signal reports were exchanged at readability 5 strength 7. When "B" relayed to "A" that contact had been established with the first link inside the cave at "C", signal report was R5 and S8. It was then suggested that "A" and "C" listen for each other, assisted by "B" as monitor, and to our amazement contact was made with signal reports of R5 and S7 to S8 each way, both "A" and "C" reporting they were copying each other better than they were copying "B". As "B" was then superfluous in the link, it was decided that "B" would make checks on signals away from the mouth of the cave, and found that signals from "C" were stronger at the foot of the slope than at the cave mouth, but as the other stations inside were in contact with each other, no check was made with "C".

Signal reports between locations "C" "D" "E" and "F" were always R5 and S8, proving that 100% reliable communications can be maintained intra Cave.

Tests made between "A" and "D" were R5 and S7, while from "A" to "F" signals were barely readable, apparently due to the narrow neck where "F" was located.

No checks were made between "A" and "E" although the signals from "A" were heard at "E".

The distance from the car station at "A" to the limestone bluff "X" (see Fig. 1) was about 1,000 feet and a further 700 feet of limestone between this point and the interior of the cave. Although no cross bearings were made, it appears that signals were received through the limestone rather than by ducting effects through the cave entrance, which the sketch (Fig. 1) shows was very well shielded in direction of the base station. Peaking the signals by use of the three element beam gave a definite indication that they were being received in a direct line and not by reflection from the surrounding cliffs.

The second experiment was made from the Orient Cave, which is one of the tourist caves, and is very much different in layout to the Glass Cave. The entrance to the Orient Cave is through a 380 foot tunnel, 8 feet high by 3 feet 6 inches wide (see Fig. 3) to a small cavern "D".

Then through a companionway 7 feet high by 2 feet 6 inches wide, being covered on top and both sides with a 1/2 inch wire mesh for a distance of twelve feet opening into the main cavern "B", which is 50 feet high.

The mobile station was located in a car "A" (see Fig. 3) about 400 feet below the top of the mountain and 50 feet from the start of the limestone slope, which rose at an angle of 60 degrees to the horizontal. All stations were within 10 feet of the same horizontal datum.

The portable unit was the crystal-controlled walkie-talkie with a quarter wave whip antenna and approx. 0.4 watt input to the final. Checks were

THE GLASS CAVE



Fig. 2

* 69 Taylor Street, Bankstown, N.S.W.

made in the tunnel where signals averaged R5 and S5. From the small cavern "D" signal strength increased to R5 and S7, and upon entering the wire mesh covered companionway, signals were completely inaudible. However, in the main cavern clear of wire mesh and guard rails, signals were exchanged at R5 and S8. The distance between "A" and "B" in a direct line was 580 feet, while the walking distance from the entrance of the tunnel to location "B" was 660 feet.

Directional checks made from the car "A" during the transmission periods from inside the cave showed a shift of up to 50 degrees away from the mouth of the tunnel when checks were being made from cavern "D", and a change of 20 degrees back towards the tunnel entrance when transmissions were made

determining the refraction of signals through the limestone and more accurately determining the path of signals.

It would appear that very good use could be made with v.h.f. links in cave search and rescue work, the exploration of cave systems, also the exact pinpointing of certain areas inside the caves by using mobile units with directional antennae located at various positions outside. These points will be investigated on the next expedition.

Sidelights of the trip were the night spent by VK2HL, VK2NP, VK2VL, and VK2AT0 when the deep freeze set in and it snowed, while they were prepared for only a summer's night; a trip through a light snow storm by VK2XX, VK2APQ, Cee. Cronan and Darrel Price when the contact with VK2HL was possibly the first mobile contact on 144 Mc.

ORIENT CAVE

SCALE 1 INCH = 40'

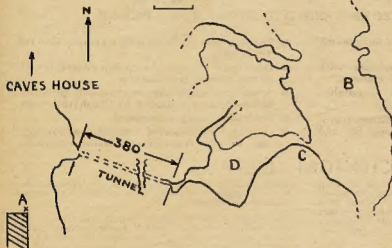


Fig. 3.

from the main cavern "B". It was noted that strongest signals were received by both stations when the portable unit operated from "B" and "D". An important point in these checks was that in the large cavern "B" signals were very much stronger than in any portion of the narrow tunnel despite the 100% increase in distance.

The limestone outside the marked section of Fig. 3 is solid and uniform, therefore it seems certain that signals were received over the direct path rather than by ducting through the tunnel.

As it was getting late in the day, and it was about 120 miles' trip back to Sydney, further tests could not be made. However, a further test is already being planned when cross bearings will be taken, together with checks on top of the mountain immediately above the caverns, with the view of

I wish to acknowledge with thanks and appreciation the co-operation of Brian O'Brien, B.Sc., President of the Sydney University Speleological Society, in arranging for these tests to be made, and for the assistance in the preparation of notes and maps for this article. Also to Mr. Best, the Director of the N.S.W. Government Tourist Bureau, and Mr. Finney, Superintendent of the Caves, for the help and co-operation they have rendered in making these tests possible.

† 88 Arthur Street, Homebush, N.S.W.

"WILLIS" CHASSIS PUNCHES



Manufactured especially for the Radio and Electrical Engineer and Constructor. Gives that clean cut professional appearance.

3/8" ...	21/-	1-3/8" ...	32/6
1/2" ...	22/6	1-3/16" ...	35/-
5/8" ...	22/6	1-1/4" ...	47/6
11/16" ...	23/6	1-1/2" ...	47/6
3/4" ...	24/6	2" ...	62/6
1" ...	31/6		

Special Sizes Made to Order.
Made of Finest Quality Tool Steel.
Guaranteed 10,000 Holes.

BRITISH "Q-MAX" SCREW TYPE CHASSIS CUTTERS

5/8" ...	24/2	1-3/4" ...	38/4
3/4" ...	24/2	2-3/32" ...	62/6
7/8" ...	26/8	1-1/4" ...	62/6
1" ...	31/8	1" Square	47/11
1-1/8" ...	31/8		
1-1/4" ...	31/8	Spare Keys	
1-3/8" ...	35/-	All Sizes ..	1/6
1-1/2" ...	35/-		

The Ideal Chassis Hole Cutter where equipment is already mounted.

"Q-MAX" GRID DIP OSCILLATOR

MODEL GDO-1A

The "Q-Max" Model GDO-1A is a high frequency grid dip oscillator with a built-in mains power pack.

FREQUENCY RANGES

"A" 1.5 - 2.9 Mc.	"B" 2.9 - 5.6 Mc.
"C" 5.6 - 10.5 "	"D" 10.5 - 20 "
"E" 20 - 39 "	"F" 39 - 75 "
"G" 75 - 175 "	"H" 150 - 300 "

APPLICATIONS

- Determination of the resonant frequency of tuned circuits.
- Tuning transmitter circuits without the application of power.
- Determination of coil, mutual and stray inductances.
- Determination of the capacitance of condensers, both fixed and variable, together with circuit and stray capacitance.

PRICE (Amateur Net):

£25/-
plus 12½% Sales Tax

House of High Quality Products.

WILLIAM WILLIS
& CO. PTY. LTD.

428 BOURKE ST., MELB'NE

Phone: MU 2426

MODEL "1XA" CRYSTAL MICROPHONE INSERT



AUSTRALIAN MADE — — FOR AUSTRALIAN CONDITIONS



FITTED WITH PLATED REAR SHIELD TO ELIMINATE HUM PICK-UP

- Patented crystal unit guarantees outstanding efficiency and performance.
- Protected against ingress of moisture with approved moisture sealed crystal element.
- Small — compact — lightweight — durable.
- Will not blast from close speaking.
- Precision engineering ensures realistic reproduction and high output with long life and dependable operation.

- The only unit available with a genuine sintered metal filter.
- Good high frequency response ensures excellent speech reproduction.
- Aluminium diaphragm mechanically protected and frequency controlled by "Zephyril" filter.
- Australian made throughout.
- Only carefully selected cements used throughout, to suit Australian climatic conditions.

TECHNICAL DETAILS

Rochelle salt crystal microphones are perhaps the most widely used for all types of service where quality speech and music reproduction at high output levels is a requirement. They are dependable in performance and when fitted with the appropriate "Zephyril" filter, their frequency response may be adjusted to suit any application or requirement.

This crystal microphone requires to be terminated with a high value parallel load of the order of 1 to 5 megohms for best results.

The mass of the moving parts is small, hence the sensitivity is high and a high efficiency is achieved.

Light gauge solder lugs are provided so that excessive heat in soldering will not be transmitted to the crystal element.

When mounted in a microphone cage, it is recommended that the insert be suspended in rubber, to eliminate shock and vibration.

One of the connecting lugs is directly connected to the case and care should be taken to solder the metal shield of the microphone cable to this solder lug, keeping the unscreened portion of the centre conductor as short as possible to eliminate hum pick-up.

All crystal elements are mounted on high grade suspension pillars, being fixed thereto with a good quality cement, thus ensuring stability and long life.

Case 1½" diameter (rear), 1" thickness, 1-13/16" overall diameter (front) with filter fitted.

Frequency Response = 60-8,500 c.p.s.
Output Level = -45 db (0 db = 1 volt/dyne/cm²)
Impedance = Model 1XA Grid 1 — 5 megohms.



Approximate Frequency Response Curve

AVAILABLE FROM ALL LEADING TRADE HOUSES

ZEPHYR PRODUCTS PTY. LTD.

58 HIGH STREET, GLEN IRIS, VIC.
(Box 2, Armadale P.O., Vic.) Phone: BL 1300

Transformer Theory and Practice

PART TWO

BY V. J. McMILLAN,* VK2AWN

Copyright. All rights reserved.

At this point we must consider another aspect of modulation transformers and that is the provision of, and reason for, the air gap in the iron circuit.

If you can remember the fundamental theory dealing with direct current solenoids, you will recall that the magnetic flux, produced in a core, is a function of turns and current flowing through the turns. Forget for a moment that our modulation transformer is a transformer, and look on it as a direct current solenoid wherein the turns are the secondary turns of the transformer, and the current flowing is the direct current supplied to the transmitter. We thus have all the elements of a direct current solenoid, i.e., turns, current flowing and an iron core. Under these conditions the total flux generated in the core is only limited by the value of ampere turns, and the magnetic reluctance of the core. In a core which is built up of overlapping laminations (which is the normal way to build a transformer) the magnetic reluctance is very low and so the total magnetic flux in the iron circuit is high. If we introduce a definite air gap in the magnetic circuit, the reluctance of the magnetic circuit is increased. The actual increase depends on the length of the air gap.

We thus have a means of controlling the initial flux density in the core due to the magnetising effect of the steady direct current.

The saturation value of transformer steel is usually of the order of 20,000 lines per square centimetre. Our modulation transformer must be so designed that at maximum signal input the saturation value of the steel is not exceeded.

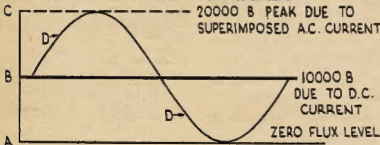


FIGURE 4.

ceeded. If we attempt to go beyond the saturation value, the excess signal input to the transformer primary does not appear on the secondary side.

Without going into the mathematics of the theory, it is sufficient to state that the initial direct current flux density in the core must not exceed 10,000 lines per square centimetre. Under this condition, the maximum flux density in the core with 100% modulation, does not exceed 20,000 lines per square centimetre.

Fig. 4 shows a familiar curve. It is more familiarly known to Radio men as the "modulation envelope" where the "A" line represents zero carrier,

"B" is steady-state carrier without modulation, and "C" is peak value of the modulating signal "D".

Fig. 4 actually shows the flux conditions in the modulation transformer core.

"A" in this case shows zero flux.

"B" is the level of steady-state flux due to the direct current supplying the r.f. carrier.

"C" is the level of peak flux reached in the core when subjected to the modulating flux "D".

"D" is, of course, the actual signal in terms of a.c. voltage.

The reason for the air gap in the core of a modulation transformer should now be quite clear. The point now arises—how do we calculate the required air gap? There are several ways to do this, but the easiest way, in the opinion of the writer, is to neglect the reluctance of the iron core itself and simply calculate for the air gap alone. That is to say, we assume that the core requires no magnetising current, the air gap requiring the lot! This assumption is not as screwy as it sounds since the greater part of the total magnetising current of a transformer is required for the air gap. This leads to a very simple calculation for the air gap, viz.:

$$\text{Air gap in inches} = \frac{0.71 \times A \times N}{B} \quad (e)$$

Legend:

B = Flux density in lines per square cm.

A = Amps.

N = Secondary turns on transformer.

0.71 = A constant.

20000 B PEAK DUE TO SUPERIMPOSED A.C. CURRENT.

10000 B DUE TO D.C. CURRENT
ZERO FLUX LEVEL

In our previously considered 60 volt-amp. transformer, let us assume that the secondary voltage is 1840. Since the secondary voltage is 487, we find that the core section will be about 1.41 square inches (net) for a flux density of 14,100 lines per square centimetre at 50 cycles. We have previously considered that it is carrying a transmitter load of 0.1747 amps. direct current. From (e), therefore, we find that the air gap under these conditions will be:—
$$0.71 \times 0.1747 \times 1640 = 0.0144 \text{ inches}$$

The value obtained by this calculation is only approximately correct, but it does show whether the air gap figure is practicable or impossible to attain. The actual air gap must be adjusted by testing the completed unit at a voltage, current and frequency corresponding to the values substituted in formula (e). Incidentally, it is most important that, for the purpose of formula (e), the frequency assumed to determine the value of "B" is the lowest frequency it is desired to reproduce. (In our example we took 50 cycles as being the lowest frequency.)

We have yet to consider the required turns ratio of our modulation transformer. Let us assume that we wish to use a pair of 807s in AB2 to provide the necessary 60 watts of power. We require to know what d.c. voltage and current they will need to provide this power. From these figures we can determine the turns ratio of our modulation transformer.

Power output calculations are somewhat involved and require a knowledge of factors which are not readily available to the average Amateur. However, the following formulae will give the required information with a reasonable degree of accuracy for class AB2 operation. The formulae do not apply to triodes.

$$\text{Power Output (W)} = \frac{E \times I \times \text{Efficiency}}{2} \quad (f)$$

$$\text{Transformer plate to centre tap voltage (V) (in r.m.s. alternating current value)} = \frac{W}{I \times 1.11} \quad (g)$$

$$\text{Plate to plate impedance (Zp) (in ohms)} = \frac{(W)^2}{I^2} \quad (h)$$

$$\text{Legend:}$$

E = Direct current applied voltage.
I = Direct current supplied to the anodes.

W = Power output in r.m.s. watts.
1.11 = A constant.

In our example we require 80 watts of output from the modulator.

From published data on 807s in AB2 service, we know that the maximum anode(s) current is 0.24 amps. The efficiency we also know will vary from about 50% to 66%, depending on applied anode voltage and permissible distortion. From our knowledge of these facts and the use of formula (f), we find that an applied anode(s) voltage of 450 volts should be suitable, since:—

* 58 Waters Road, Naremburn, N.S.W.

From formula (e)
 $450 \times 0.24 \times 55.5\% = 60 \text{ watts.}$

The plate to centre tap applied voltage will be—
 From formula (g)

$$\frac{60}{0.24 \times 1.11} = 225 \text{ volts (r.m.s., a.c.)}$$

The plate to plate impedance will be—

$$\text{From formula (h)} \\ \frac{[2(225)]^2}{60} = 3375 \text{ ohms}$$

We do not actually require to know the plate to plate impedance, but the author has shown the calculation as a matter of interest.

As shown above, the plate to centre tap voltage is 225 volts. Obviously the plate to plate voltage is twice this value, that is, 450 volts.

Referring back to our example, we said that the transformer was modulating a transmitter load of 600 volts and 0.1747 amps. Since we cannot exceed 100% modulation (without taking steps to avoid splatter), the peak a.c. voltage which we can apply to the carrier must not exceed the d.c. voltage. Since all transformer calculations are carried out on the basis of r.m.s. values, we must convert the peak value of voltage to a r.m.s. value, viz.:

$$600 \times 0.707 = 424 \text{ volts r.m.s.}$$

This 424 volts is the actual voltage we require across the load, but as we have seen, we must make allowance for the internal resistance drop of the transformer (at low frequencies).

As was previously mentioned, the actual load is 3435 ohms plus an additional effective transformer resistance of 148 ohms. The total no-load secondary voltage must therefore be—
 $424 \times (3435 + 148) = 443 \text{ volts approx.}$

3435

We assumed that the secondary had 1640 turns on it, so that the total primary turns must be—

$$\frac{1640 \times 450(V)}{443(V)} = 1668 \text{ approx.}$$

A centre tap must be brought out at 834 turns.

Most of the calculations are now completed for our modulation transformer. One thing you will note is that the start of all calculations springs from the known required output voltage and current. On these small transformers it is usually sufficient to base the required output on the actual load plus 10% (for transformer losses). The required primary turns is the last item to be calculated.

The only factor we have not yet considered is—how to predetermine the transformer leakage reactance.

TRANSFORMER LEAKAGE REACTANCE

There are many formulae used to predetermine transformer leakage reactance. Every transformer manufacturer has his own pet theories on this subject. For our purpose we will only consider one which is applicable to our particular case, viz.:

$$\%X = \frac{A.T. \times M.T. \times (A + B + 3C) \times F}{S \times 3 (A.L.) \times V.T. \times 50 \times 1000}$$

where: (k)

A.T. = Total secondary ampere turns.
 M.T. = Mean length of leakage space in inches.

A = Effective depth of primary winding in inches.

B = Effective depth of secondary winding in inches.

C = Space between primary and secondary in inches.

S = Number of winding sections.

A.L. = Winding length plus (A + B) ÷ 3 (approx.) in inches.

V.T. = Volts per turn.

F = Frequency.

50 = A constant.

1000 = A constant.

This formula only applies to a transformer that has the primary and secondary windings arranged concentrically, i.e. one wound over the other.

We will consider, as an example, a transformer rated at 5000 volt-amps. (5 kVA.) single phase, 50 cycles, with one primary and one secondary coil, and a voltage ratio of 240/480 volts. At 5000 volt-amps. rating the secondary (480 volt) current will be—

$$\frac{5000}{480} = 10.42 \text{ amps. (approx.)}$$

The primary turns are 178 and the secondary turns 356. The coil dimensions, shown as a centre line section in Fig. 5 (all dimensions in inches) are:—

A = 0.36 inches

B = 0.84 inches

C = 0.33 inches

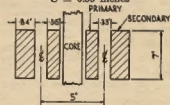


FIGURE 5.

Assuming that the coils are wound on round cylinders, the value of "M.T." in formula (k) will be—
 $5" \times 3.14" = 15.7 \text{ inches approx.}$

The value for "A.L." in formula (k) will be—

$$\frac{7" + 0.36 + 0.84}{3} = 7.4 \text{ inches}$$

The value for "A.T." in formula (k) will be—
 $356 \text{ (turns)} \times 10.42 \text{ (amps.)} = 3710 \text{ approx.}$

The value for "V.T." in formula (k) will be—

$$\frac{480 \text{ (volts)}}{356 \text{ (turns)}} = 1.35 \text{ approx.}$$

The value for "S" in formula (k) will be 1 in our example since there is only one winding group. In general, the number of winding groups can be taken as the number of separate spaces between primary and secondary coils. More of this later.

We now have all the information necessary to determine the percentage leakage reactance of this transformer at 50 cycles.

From formula (k):—

$$\begin{aligned} \%X &= \frac{3710 \times 15.7 \times [0.36 + 0.84 + 3(0.33)] \times 50}{1 \times 3(7.4) \times 1.35 \times 50 \times 1000} \\ &= \frac{3710 \times 15.7 \times 2.19 \times 50}{1 \times 22.2 \times 1.35 \times 50 \times 1000} \\ &= 4.26\% \text{ approximately.} \end{aligned}$$

Fig. 6 shows the same transformer except that the windings have been arranged in a fashion that is technically known as double concentric. In this arrangement one half of the primary winding is wound inside the secondary winding and the other half is wound outside the secondary winding. (Incidentally the terms primary and secondary in this sense can be changed over without affecting the operation in any way.)

This arrangement of windings reduces the leakage reactance to a remarkable degree. Formula (k) still applies, but the values change considerably, viz.:

A.T. remains the same.

M.T. now becomes the average of

$$(5 \times 3.14) \text{ and } (7.34 \times 3.14) = (15.7 + 23.1) \div 2 = 19.4 \text{ inches.}$$

The values of A and B are now only one half of what they were before, that is, 0.18 and 0.42 respectively.

The value of S now becomes 2 because there are two winding groups.

The value of A.L. becomes slightly less, viz.: $7 + [(0.18 + 0.42) \div 3] = 7.20 \text{ inches.}$

The value for A + B + 3C now becomes: $0.18 + 0.42 + 3(0.33) = 1.59.$

All other values remain the same so that we can substitute the values in formula (k) and obtain:—

$$\begin{aligned} \%X &= \frac{3710 \times 19.4 \times 1.59 \times 50}{2 \times 21.6 \times 1.35 \times 50 \times 1000} \\ &= 1.96\% \text{ approximately.} \end{aligned}$$

We can thus see that, in the particular example quoted, we have reduced the leakage reactance to something less than 50% of what it was originally.

If the space between the primary and secondary coils is small as compared with the winding depth, the reduction in leakage reactance is even more marked.

Fig. 7 shows the same transformer with the windings arranged double concentrically and, in addition, the windings are divided over two legs of the core.

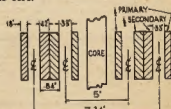


FIGURE 6.

The values to insert in formula (k) now become:—

M.T. is the average of (5×3.14) and (6.5×3.14) , which is $(15.7 + 20.4) \div 2 = 18.05 \text{ inches.}$

The values of A and B as shown in Fig. 7 are 0.09 and 0.21 respectively.

The value of S now becomes 4 because there are four winding groups (or 4 spaces between primary and secondary coils).

The value for A.L. becomes: $7 + [(0.09 + 0.21) \div 3] = 7.1 \text{ inches.}$

The value for A + B + 3C now becomes: $0.09 + 0.21 + 3(0.33) = 1.29.$

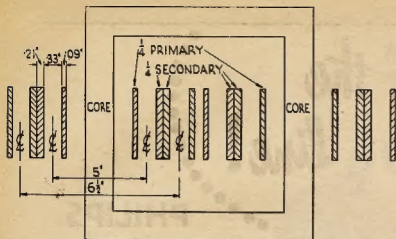


FIGURE 7.

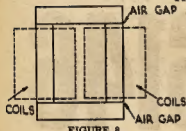


FIGURE 8.

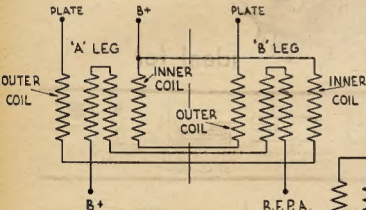


FIGURE 9.

Since all other values remain the same, we can now calculate from formula (k):—

$$\%X = \frac{3710 \times 18.05 \times 1.29 \times 50}{4 \times 21.3 \times 1.35 \times 50 \times 1000} = 0.75\% \text{ approximately.}$$

Fig. 8 and Fig. 7 shows the mean diameter of the first primary to secondary space constant at 5 inches. In actual fact this dimension would become progressively smaller if we maintained the same clearance to the core. The reactance values shown for Fig. 6 and Fig. 7 would, therefore, be somewhat less than those shown.

From the point of view of reducing reactance to obtain a good high frequency response in modulation trans-

formers, obviously the arrangement shown in Fig. 7 has the most merit. From an Amateur constructor's point of view, this type of construction lends itself to practical manufacture.

Fig. 8 shows a modulation transformer core built up of four "I" pieces of suitable length to suit the coils as wound. Note that the air gap is in four sections so that if we wish to obtain an air gap of 0.0144 inches [as calculated from formula (e)], each gap must be $0.0144 \div 4 = 0.0036$ inches approximately.

The completed core must be tightly clamped together with non-magnetic clamps (brass, wood or bakelite, etc.).

It is a good idea to make a containing case of flat iron (galvanised will do nicely), nearly fill it with molten paraffin wax, then immerse the completed transformer in it. When the wax solidifies, you will have a transformer that is free from "talk back" and, at the same time, you will have a transformer that is repairable if you are unfortunate

enough to have a winding or insulation failure.

There is just one further point in building a modulation transformer to this general arrangement, and that is, that the windings must be properly interleaved in the arrangement of connections. Fig. 9 shows the correct connections for all coils. The winding direction must, of course, be such that series connection is obtained in the coil groups. This arrangement ensures the same percentage resistance and reactance between each half of the primary (taken separately) to the secondary, and also a low value of leakage reactance between each half of the primary winding.

Fig. 10 shows a coil grouping arrangement which has a still lower leakage reactance between halves of the primary winding whilst at the same time having the other advantages claimed for Fig. 9.

CONCLUSION

The foregoing article represents the views of a Power Transformer Designer on modulation transformer problems. I have no doubt that there are better qualified Institute members on this subject.

Certain approximations have been used in order to simplify the approach to the problem. I hope that the article will be of some practical use to those keen types who like to build their own equipment.

I further hope that those of you who are using radio power transformers as modulation transformers will see the error of your ways! You cannot expect a high fidelity signal if your modulation transformer is not properly designed, irrespective of how good your microphone or amplifier equipment is. If you are happy with communication quality, OK, but if you want a high quality signal don't waste your time using an inferior modulation transformer.

If you don't feel like building one, buy the biggest and best transformer you can afford. The old adage about

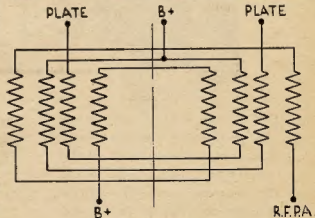


FIGURE 10.

"good things coming in small parcels" does not apply to modulation transformers. If you have to decide between two commercially made units of about the same price, buy the heavier of the two units and you won't go far wrong.


Hot off the production line!

PHILIPS

TYPE

6146

ideal for

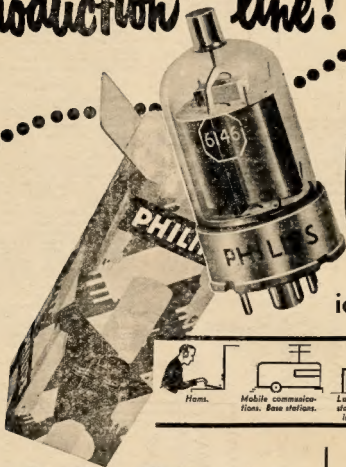

Homs.



Mobile communications.
Base stations.



Low frequency
stages in broadcast-
ing transmitters.



Medium to high
power PA systems.

THE versatility of Philips type 6146 tube has already made it famous overseas. Check its performance and you'll see why! Under I.C.A.S. conditions a pair in class AB1 will give 120 watts of audio—and it's an efficient tube up to 175 MCs. The wide range of applications of the Philips type 6146 makes it a tube to remember!

Write for
information
and data
sheets



**PHILIPS
ELECTRICAL INDUSTRIES
PTY. LTD.**

69 Clarence St., Sydney, N.S.W.
590 Bourke St., Melbourne, Victoria
148 Edward Street, Brisbane, Qld.
381-S Murray St., Perth, W.A.
119 Grenfell St., Adelaide, S.A.

Bandspredding the Super-Pro on all Bands

BY RON HENDERSON,* VK3ARV

ONE of the most popular receivers ever to grace the Amateur's table or rack-type layout is the Australian-made version of the Hammarlund Super-pro receiver, with which I think every Amateur and S.W.L. is familiar. These receivers have been popular for many years now and give good service if treated properly and operated correctly. With the conclusion of hostilities, these receivers were released on the Melbourne market. Although only very few completed receivers were taken by the U.S. Army, plenty of bits and pieces were obtainable to build your own receiver if you so desired.

From a bare chassis the receiver was built up, coils wound, adjusted and finally calibrated. Many hours were spent at first enjoying the fruits of labour in listening to the new receiver, which looked like a first-class receiver at last to grace the shack table.

In those days we had the full span on the 7 Mc. band to listen to and somewhat crowded conditions of the Sunday morning doggies of QRM made tuning rather critical, owing to the capacity on the bandspread dial being larger than I thought would be necessary. After some thought, a scheme was evolved whereby full bandspread was possible on all bands including eighty metres. This was not built into the original design of the Super-pro and the following method is a delight to use on the crowded bands. With intelligent use of the crystal filter and phasing control, any signal can be copied with ease, on the extended bandspread system adopted.

Major alterations are not required, nor is the receiver taken apart for it is practically a wrecking job to remove the coil box from the chassis, not to mention the re-wiring job which would probably frighten most of you into turning over this page. All that is required is the removal of the two top plates over the bandspread tuning condensers as well as the main tuning condenser. It is necessary to use an extended tip on the soldering iron to reach the coil contacts.

First of all locate the small section of the bandspread gang that connects to the 15 to 30 Mc. coils, remove this connection and run an insulated wire, preferably 16 gauge, across the top of the coil-contact finger board and solder to the connection of the main tuning condenser on the contact board in that stage. Feeding the wire across the board is not hard with long nose pliers. This by-passes the switch and is a permanent connection. Repeat this operation on all stages—R.F., Mixer and Oscillator. With careful use of the soldering iron down past the main gangs no damage will result and you will find that this will not alter the range covered on the 28 Mc. band, nor the new band of 21 Mc. covered on the same coils. This connection will also be satisfactory for the 14 Mc. band on the 10-20 Mc. coils.

Now remove the connection to the contact board of the 10-20 Mc. coils and repeat this operation on all stages as before, bandspread gang only, of course, then remove the connection to the 5-10 Mc. coils of the larger gang and solder this lead to the eighty metre coil range, 2.5-5 Mc. in other words. Move this connection along one solder lug, now connect the 10-30 Mc. gang to the 5-10 Mc. coils on all stages and you will find your task is completed.

Before replacing the two small top plates above the respective gangs, go over your connections and re-read this article if necessary.

Placing the bandspread dial on minimum capacity, make a run over the frequency of your receiver with an accurate signal generator, Bendix frequency meter or what have you, to see if the shifted wires have upset the calibration of the receiver on the 15-30 Mc. band as well as the 10-20 Mc. band. Some slight touch up in calibration may be necessary on these two bands. If more than 500 Kc. out, something is wrong, but don't give in yet, you may still have room to move the trimmer on the high end of the band and the slug at the low end to put things in order


broadcast or 7 Mc. band that is covered by this range of 5-10 Mc.

We now tackle the 2.5-5 Mc. range and with the bandspread dial still on minimum capacity as before, make a run over the range that is covered by these coils and check with your Signal Generator to see if the lead capacitance or inductance has made much difference to your calibration, although not much difference should be noticed on this band, and the trimmers and slugs can be touched up as before.

On the 3.5 Mc. band the main tuning condenser is set to 3.96 Mc. and it is now a pleasure to work other stations with the generous bandspread. Almost 80 divisions is used to cover this band, whereas previously you had no bandspread at all.

For those lucky chaps who work 7 Mc. phone DX, the main tuning condenser is set for 7.3 Mc. and you will now have at least 85 divisions to chase the elusive DX on this band. For the range of the 150 Kc. allotted to us for this band, 45 divisions will be available, more than ample for the average and certainly well worth the trouble. On the 14 Mc. band, use almost the full scale of the bandspread dial.

OLD METHOD

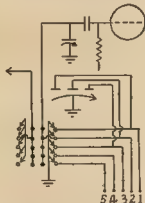


NEW METHOD

Switch Shown
IN Position 2.

RANGES.

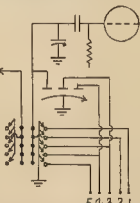1. 15 to 30 Mc.
2. 10 to 20 Mc.
3. 5 to 10 Mc.
4. 2.5 to 5 Mc.
5. 1.25 to 2.5 Mc.



again, if not, you have extra lead capacitance. You will probably find it is the lead from the small section of the bandspread gang which is connected to the main gang, that is the culprit. It should be spaced from the other wires on the switch by at least half an inch.

If you were as fussy as I was you will find that by using solid copper wire (insulated), for the oscillator stage, most of your frequency drift will have disappeared. The 5-10 Mc. coils will now need checking as we now have both the small sections of the gang in parallel across the coil and although not much difference in lead length is noticed, the change in position of these wires may upset the calibration just a small amount, but only a few hundred kilocycles at the most.

We now have less capacitance across the coil. This will increase the coverage on the required band, whether it be the

The writer will be pleased to answer any queries regarding this article if you will be good enough to include a stamped addressed envelope for reply. The writer has now almost finished his second Super-pro receiver in order to chase two signals at the one time, very handy for contest work. Many of these receivers have been serviced and the bandspread system altered as described, much to the satisfaction of everyone.

The circuit diagram included only shows one stage altered as given in the instructions, the same connections will, of course, be carried out on all four stages in the Super-pro.

For those people who listen on the broadcast band, 1.25 to 2.5 Mc., the bandspread dial will have to be placed on zero or minimum capacitance for the calibrations to read correctly because there is approximately 10 pF permanently connected all the time.

* 18 Mudden Grove, Burnley, E.I. Victoria.

Eighth Annual Urunga Convention

The Eighth Annual Urunga Convention will be held over Easter Week-end, 30th March-2nd April, and the organisers are looking forward to your support to make this the best Convention ever held at Urunga, or for that matter at any place!

V.h.f. enthusiasts will be interested in the two metre mobile and blindfold transmitter hunts, whilst the h.f. men can take part in the 40 metre battery-operated Gerry Challenger Memorial Contest and the all-band scramble with phone from any place they can get it. Fishing enthusiasts and tall story tellers may even come up for prizes, too.

Accommodation is available at the Ocean View Hotel and several guest houses, whilst we can provide stretchers under shelter for those who wish to fend for themselves.

Accurate tariff figures are not available at the moment, but last year the

hotel was 35/6 per day, the guest houses 25/- per day with cheaper rates per week.

You are strongly recommended to book your accommodation now by writing to VK2AHH at Kempsey, stating type of accommodation, number of persons, date and time of arrival and departure, and enclose £1 deposit per person.

The area is served by train, whilst arrangements can be made to pick you up at Coff's Harbour if you elect to come by plane.

Our Sunday night concert is of the highest standard and the pleasure of meeting your old coppers and making new friends are two further attractions to bring you to Urunga.

SO DON'T FORGET URUNGA.

MARCH 30 TO APRIL 2.

—N. A. Hanson, Nth. Coast Zone Officer.

This book has been written especially for those radio servicemen who, having a sound knowledge of circuit fundamentals, wish to prepare themselves for t.v. servicing.

Several chapters are devoted to the theoretical explanation of scanning, the operation of the picture tube and the wave form of the actual t.v. signal. Next comes a detailed description of a modern t.v. receiver, and to aid the discussion the entire circuit diagram is included. Such problems as antenna matching and r.f. amplifier design are fully covered.

A description of various types of portable test instruments is given, including a pattern generator and t.v. signal tracer.

The final one hundred pages are devoted to a series of illustrations, showing the picture as it appears when the receiver is incorrectly adjusted, or some component part is faulty. Each is shown with firstly the test pattern from the t.v. station and then as it appears using a t.v. pattern generator as the signal source.

This book should be a very welcome addition to any Amateur or Serviceman's book shelf.

There are 264 pages, 6" x 8½", cloth bound.

Our copy by courtesy of Philips Electrical Industries (Aust.) Pty. Ltd. Price in Australia is 40/-.

50 Mc. W.A.S.

Call	Cor. Add. No. Conts.	Call	Cor. Add. No. Conts.
VK3WJ	12 4	VK2AEZ	10 1
VK3WP	8 3	VK3XA	11 1
VK3WV	9 2	VK3OM	12 1
VK3WY	3 2	VK3ACL	14 1
VK3HR	4 2	VK3ZD	16 1
VK3LC	1 1	VK3HO	17 1
VK3DF	3 1	VK3ADC	1 1
VK3RE	6 1	VK3WH	12 1
VK3HT	7 1		

BOOK REVIEW

"INTRODUCTION TO T.V. SERVICING"

By H. L. Swallow and J. v.d. Weerd

With the advent of t.v. in this country in the very near future, the addition to the Philips Technical Library of a comprehensive volume on t.v. servicing is very welcome.

SPECIAL

BRIGHT STAR RADIO are pleased to announce an addition to their line of Crystals. We are now manufacturing—

VACUUM MOUNTED CRYSTALS

for general communication frequencies in the range 3 to 14 Mc.
Higher frequencies can be supplied.

ADVANTAGES OF THIS TYPE—

- (1) Approximately three times the activity of normal plated crystal due to the absence of air damping.
- (2) Better frequency stability due to the absence of air friction.
- (3) Plating cannot deteriorate with time and cause frequency shift.
- (4) Two or more crystals can be mounted in the one envelope and thus save space.

Price depends on the tolerance and frequency required, and will be quoted upon request.

BRIGHT STAR CRYSTALS may be obtained from the following Interstate firms: Messrs. A. E. Harrold, 123 Charlotte St., Brisbane; Gerard & Goodman Ltd., 192-196 Rundle St., Adelaide; A. G. Healing Ltd., 151 Pirie St., Adelaide; Atkins (W.A.) Ltd., 894 Hay St., Perth; Lawrence & Hanson Electrical Pty. Ltd., 56 Collins St., Hobart; Collins Radio, 409 Lonsdale St., Melbourne; Prices Radio, 5-6 Angel Place, Sydney.

BRIGHT STAR RADIO

46 EASTGATE ST., OAKLEIGH, S.E.12 UM 3387



Further Notes on the Transmitter with Low Harmonic Output

BY H. F. RUCKERT,* VK2AOU

This series of articles have created some interest among members and the author would like to give further information in reply to the many questions received.

We have to start, unfortunately, with the correction of a few errors:

(1) The four-range switch under the v.f.o. (October "A.R." page 2) is used to switch the filaments of the multiplier stages off which are not in use. It actually would not matter if they were on all the time. The different resistors in the plate, screen and cathode circuits of these stages limit the current enough not to cause damage when the v.f.o. is not delivering r.f. The same applies to the 807 driver.

(2) The five links, coupling to the tuned grid circuits of the driver 807, should not be connected to the cold ends of the grid tuned circuits. They are directly grounded. The tuned circuits are by-passed at their common cold end with a 0.01 μ F. to ground. The 25,000 ohms grid leak resistor must not be shorted out (Oct. "A.R." page 3).

(3) The upper link of the 807 plate multiband circuit should be grounded in a similar way to the lower link. The centre lead must not be grounded.

V.F.O. NETTING

VK2AHH, being an excellent observer, caught the author by saying: "How can a shielded v.f.o. give a beat note in a receiver when the p.a. or doublers are not working?"

The answer: The transmitter is not as well shielded as a signal generator should be. The receiver is next to the transmitter and is connected to the transmitter at the antenna relay and the stand-by relay, and uses also the same mains line. The v.f.o. gives only a S3 signal in the receiver, whilst a grid dip meter gives S9 plus 40 db. (no aerial); the BC221 gives S9 (no aerial).

The second station receiver's first oscillator gives S9 plus 25 db., therefore the shielding of the transmitter is not so bad after all, and t.v.i. cannot be expected.

The three circuit band-filter at the grid of the driver was the best way to prevent long leads with high impedance and high r.f. voltage going to the driver from the different multipliers. We also prevent, in this way, detuning of multiplier circuits because they are not switched on to different leads and valves with different capacities.

The two ranges of the v.f.o. work like this: The whole 3.5 and 28 Mc. bands can be tuned with the 25 pF. air capacitor by shorting out the 25 pF. fixed capacitor and leaving open the contact to the 12 pF. capacitor. The narrow bands like 7, 14, 21 Mc. and the c.w. part of 3.5 and 28 Mc. can be spread over the dial by putting the 25 pF. fixed capacitor in series with the air condenser and the same starting frequency—just below 1750 Kc.—is achieved by switching the 12 pF. capacitor parallel to all the capacitors.

ABSORPTION TYPE FREQUENCY

METER

Nov. "A.R." page 3, 2nd column, 5th para.: It was said that a sensitive absorption type frequency meter did not indicate any harmonics at the driver or p.a. stage. Unfortunately it remains to be discussed what is a very sensitive frequency meter of this kind? An examination of the matter had the following result:

Using two different industrial manufactured absorption type frequency meters (0.1 to 60 Mc. and 20 to 220 Mc.), which were not shielded, resulted in overloading of the other components with power from the fundamental, and the harmonics are not indicated. The frequency meter the author built himself has a sensitivity of 4 to 40 mV. link coupled from a calibrated signal generator with the 70 ohm co-ax cable, depending on the L/C ratio of the frequency meter (more sensitive with low capacity at the high frequency end of the ranges) for one scale division deflection of the 40 μ A. meter. With this meter we could detect the harmonics of the multipliers, driver and p.a. stages, and also the second harmonic of the g.d. meter and receiver oscillators.

What does this mean? If we have, for example, 800V. d.c. at the plate of the p.a., we may get 500V. r.m.s. r.f. at the tank circuit. If our absorption frequency meter reads full scale one inch away from the tank or antenna coupler circuit at any harmonic frequency, we know that we have about a few volts of harmonic energy in these circuits.

This is far too much for the international required harmonic suppression of 60 db. (1:1000).

It will not be easy to do much about this at the p.a. tank or at earlier stages. We must prevent any direct radiation from these stages by shielding and filtering out-going leads. But at the antenna coupler circuit we should only get a few mV. of the second harmonic (fundamental:harmonic = 10,000:1). Of course there should be nothing after the 50 to 70 ohm impedance low-pass filter at frequencies above 41 Mc., as far as the possibility of checking of harmonics with this frequency meter is concerned (fundamental:harmonics = 50 volts:u-volts). The remaining harmonics should not cause t.v.i. if the t.v. receiver is within a 15-mile radius of the t.v. transmitter and not behind a steep cliff shielding the t.v. signal from getting to it.

At the tank of the p.a. we can find very weak 14 Mc. harmonics up to the 15th at about 213 Mc. with this frequency meter.

CONSTRUCTION OF ABSORPTION FREQUENCY METER

A small 50 to 100 μ A. meter is satisfactory. All components must be placed in a shielded box of 2" x 3" x 5" for example. Only one coil end is insulated and the coil is plugged in outside. A good Ge diode should be used. Valves are far less sensitive and not satisfactory without an amplifier. The coupling between the tuned circuit and the rectifier,

(Continued on Page 18)

COIL TABLE FOR VK2AOU TRANSMITTER (see "A.R." for Oct. and Nov., '55)

Stages Mc.	Diam. inches	Length inches	Turns	Remarks
V.F.O. 1.75 Mc.	1.38	1.9	80	On ceramic tube.
Driver Tank Multi-Band 3.5 to 32 Mc.	1.38	1.1	10	4 turn link.
P.A. Grid Circuit Multi-Band 3.5 to 32 Mc.	0.98	1.42	23	5 turn link.
P.A. Tank, Pi-Network 28 Mc.	0.71	1.34	20	4 turn link.
One coil with 14 Mc. tap for 21 Mc.	2.3	1.54	6	1/2 inch diam. tubing.
One coil with 3.5 Mc. tap for 7 Mc.	2.77	3.16	15	1/2 inch diam. wire.
Antenna Coupler Multi-Band 3.5 to 30 Mc.	2.36	4.5	21	1/2 inch diam. tubing. With taps for scope and feeders at 2 to 8 turns
	1.78	3.0	15	100 pF. air cap in the middle. 1/2 inch diam. wire.
R.F.C. at P.A. Tank	0.79	2.37	90	Not critical, close wound. Has no resonance holes between 3.5 and 30 Mc.

Band Pass Coils: 13 mm. diam., 1 to 2 cm. long. (Short 6 mm. diam. slug for 14-28 Mc., long 10 mm. diam. slug for 3.5-7 Mc.).

Air Coils 8 inch diam. may be used and calculated from graph and formulae given in "A.R." November, 1955, T.V.I. Filter article. Use calibrated grip dip meter for aligning.

* 25 Bertille Road, Beverly Hills, N.S.W.

QRP T/R Switching for 144 and 288 Mc. Antennae

BY PHIL WILLIAMS,* VK5ZAD

The method of switching, which is described here in its simplest form, lends itself to transmitters of the 10-20 watt class, such as the 522 on 2 mx or the push-pull 7199s on 1 metre. Most suitable relays for transmit/receive facilities are quite expensive, or introduce considerable impedance irregularity in the transmission line on either transmit or receive position—sometimes both.

The only apparatus needed in this method is a 4 x 3 oak switch (mine was obtained from an English I.F.F. set) and two additional quarter wave sections of the transmission line you happen to be using. Two switch contacts are used to short these stubs while transmitting and open them while receiving, the third controls receiver h.t., and the fourth the transmitter h.t.

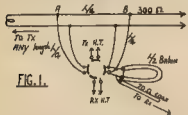


FIG. 1.—T/R switch shown in transmit position.

It will be noticed that in Fig. 1, which is drawn for the transmit position, the line from the transmitter to the aerial is direct, and only has two shorted quarter wave stubs connected to it at A and B. They do not adversely affect transmission. The balun to the receiver is shorted so that the leakage to the receiver is quite small, in fact it is less than the capacitive leakage from an

open relay contact. It is advisable, nevertheless to include a grid leak in the first stage of the receiver to bias it off while transmitting.

On switching to the receive position (shown in Fig. 2), the switch at D allows signal from the antenna to pass along the stub BD to the receiver balun and co-axial cable to the receiver input tuned circuit (not shown). The two quarter wave sections BA and AC now form a half wave line having high impedance at B and C, with the transmitter connected to the low impedance point at A. The transmitter impedance at A may be anything at all while the h.t. is not applied, and therefore connecting it to the half wave line at A effectively isolates it from the receiver circuits so that it does not affect the matching.

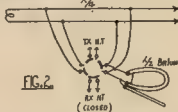


FIG. 2.—T/R switch shown in receive position.

No adjustments are required on the T/R switch itself. Simply switch to transmit and adjust the coupling and tuning for the required output conditions, then switch to receive and adjust your receiver input for best results—either max. signal or optimum noise figure if you're fussy.

Don't forget to apply the velocity correction factor to the quarter wave line sections, and the half wave balun if you use one. On 144.5 Mc. a quarter wave-

length of open wire is 20 inches long, 300 ohm ribbon is 18 1/2 inches long, and polythylene co-axial cable is 13 1/4 inches long. The balun is, therefore, 27 inches long. You may simply halve these for 288 Mc. Measure the stub lengths from the switch contacts, not the switch terminals—particularly at 288 Mc.

This scheme may be used with co-axial cable throughout, in which case the balun is, obviously, not required and switch D shorts the receiver co-ax line a quarter wave from the tapping point at B.

Somebody may like to adapt this method of switching to 5 or 10 metres, with lumped circuit elements replacing the quarter wave stubs.

TABLETOP TRANSMITTER


Next month VK2YV's transmitter will be featured. This consists of a Geloso v.i.o., 8146 (or 807) p.a., and 6L6 modulators. The complete phone and c.w. transmitter (including power supplies) is built on one chassis. The article will be illustrated with photographs.

TRANSMITTER WITH LOW HARMONIC OUTPUT

(Continued from Page 11)

etc., must not be too tight and 1 pF. bead type ceramic capacitor is recommended.

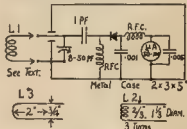The two r.f. chokes are wound on any 1 watt high ohm (100,000 ohms to 1 megohm) carbon resistor serving as a former only, with about 30 to 40 turns.



The calibration can be done with a good g.d. meter and a calibrated receiver for checking. The higher frequencies may be checked with a parallel wire Lecher system using the g.d. meter as r.f. generator. By using an 8-50 pF. air capacitor, the ranges 16-36, 36-92, and 92-235 Mc. can be covered. Coil L1 has six turns, and is slug tuned. The others are wound to dimensions given.

ANTI T.V.I. FILTERS FOR THE AMATEUR TRANSMITTER

An error appeared in this article in Nov. "A.R." on page 10 at the top of column three. The factor "m" is always smaller than 1, therefore the notations to the formula should read: "m = values between 0.6 and 0.8 (often used). In our example m = 0.65."

On page 11, first column, tenth and eleventh lines should read: "and m near 0.65."

THE LONG-AWAITED

W.I.A. LOG BOOK

IS NOW AVAILABLE

The Log Book has 96 pages—48 ruled and 48 blank. Size: 10" x 8".

There are 34 lines per page, and good quality paper is used.

★ ★

Price 4/6 plus 9d. Postage & Wrapping

★ ★

AT PRESENT AVAILABLE ONLY FROM—

VICTORIAN DIVISION W.I.A., 191 Queen Street, Melbourne, C.I.

transistors

tv

fm

audio

hi fi

ultra linear

new valves



radiotronics

1956

During 1956, "Radiotronics" will feature exclusive articles on transistors, ultra-linear equipment, T.V., F.M., Audio, Hi-Fi, and the latest information on all new valves.

Men in both the amateur and professional fields find that "Radiotronics" keeps them abreast of the latest development in the Electronic World.

Subscription: 10/-

Please do not send stamps.

AMALGAMATED WIRELESS VALVE COMPANY PTY. LIMITED

47 YORK STREET, SYDNEY, N.S.W.

VC12-56

A Mobile Transmitter and Antenna


BY R. S. FISHER,* VK3OM

The transmitter and antenna to be described are used by the writer as companion pieces to the crystal controlled mobile converter previously outlined.¹ The combination has given excellent results over the last 12 months.

THE TRANSMITTER

The transmitter operates as a medium power crystal controlled unit on the 80, 40, and 20 metre bands. It features 10 watt input, ample plate and screen modulation and provision for crystal or dynamic microphone input. With the final amplifier running 15 watts input, the entire unit draws 14 amps from a 6 volt battery. This is well within the capabilities of the average car's electrical system.

The r.f. section of the transmitter uses a 7C1 Pierce oscillator driving an 807 or 2E26 in the final. This gives plenty of drive for the final with either 40 or 80 metre crystals. For 20 metre operation it is necessary to double in the final amplifier. This does reduce the efficiency slightly, but as it simplifies the tuning considerably, it was considered worthwhile. Some adjustment of oscillator output can be had by

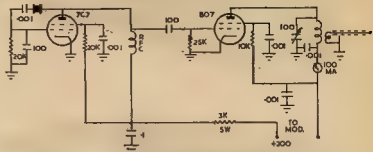

MOBILE TRANSMITTER R.F. SECTION

The modulation transformer in the original transmitter consisted of two speaker transformers back to back. The first a 10,000 ohms c.t. to 2.3 ohms, the second 2.3 ohms to 5,000 ohms. Providing medium sized transformers are used, this works very well. However, if it is possible to obtain a small modulation transformer, so much the better. The writer now uses an SCR522 modulation transformer.


gauge wire wound on a lead pencil. These are self supporting. The high tension chokes are ordinary 2.5 mH. r.f. chokes.

Two relays are needed to control the transmitter. One is connected in the main low voltage line from the battery, the second by the power supply to switch the vibrators on. This relay becomes the transmitter control.

Low voltage relays are easily obtained from motor accessory suppliers in the form of head lamp and horn relays. These will easily handle the current involved.

The best position to mount the transmitter depends on the type of car and the available space. Some positions worth considering are the luggage boot, under the dash, in the glove box, under the front seat (usually plenty of room here) and on the bulkhead.

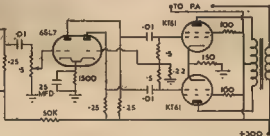The transmitter and power supply can be easily constructed on an 8 inch by 10 inch chassis. The writer has constructed his in a medium-sized amplifier cabinet. This makes a neat unit that takes up little space.




MOBILE TRANSMITTER MODULATOR

either increasing or decreasing the value of the h.t. dropping resistor. The circuit specifies a 3,000 ohm resistor which should give about 3 milliamperes drive. The final is quite straight-forward in design. It uses plug-in coils to change to the various bands. With a $\frac{1}{4}$ inch diameter former, wind on 10 turns for 20 metres, 20 turns for 40 metres, and 35 turns for 80 metres. The plate tuning condenser can be an ordinary close-coupled receiving type.

The modulator is designed to have an ample gain for any crystal or high impedance dynamic microphone. A 6S7/7 or 6AU6 preamp. drives a 6SL7 or 717 paraphase inverter, which in turn drives a pair of 6K6's in Class AB1. These tubes were used in preference to 6V6's as they take less plate current. As it is they are slightly over biased and the pair draws about 60 milliamps. Some care should be used in the layout of the modulator to avoid r.f. feedback. This is especially important with the 6S7/7 stage. Return all earth leads of this stage to a common point and then experiment for the best earthing position.

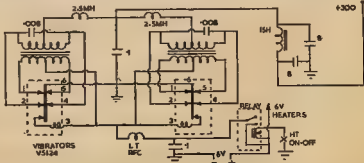The power supply uses two transformers and two vibrators. As shown in the circuit, they are wired as two separate supplies, and their input and output are connected in parallel. The transformers are rated at 300 volts 75 milliamperes. These are standard items and easily obtained. The vibrators are 6 volt standard synchronous units. The low tension chokes consist of 15 turns of 18



MOBILE TRANSMITTER VIBRATOR SUPPLY

THE ANTENNA

A mobile installation depends on its antenna. No matter how good the transmitter may be, it will be useless unless the antenna is doing its job. This, of course, applies to all types of stations, but more particularly to the mobile station. As we must work under diffi-


* 81 Neerim Road, Glenhuntly, S.E.9, Victoria.
1—"A.R.," September, 1955.

cuit conditions with a short antenna of relatively low efficiency, it is essential that we use every watt of power in the best possible way.

The design of the mobile antenna is often looked upon as being the most exacting part of putting together a complete mobile set-up. In actual fact, its construction is probably the easiest part of the whole thing.

DESIGN FACTORS

Let us start with a description of just how a short whip antenna works on the lower frequencies. Its operation is, of course, based on a quarter wavelength antenna working against ground, the ground in this case being the car body. On ten and fifteen metres this can be done, as a quarter wave on these bands is eight and twelve feet; it is possible to feed a whip of this length with fifty ohm co-ax as it stands.

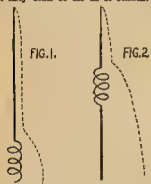

Current flow Bottom & Centre loaded

As the frequency is lowered it becomes impractical to put an antenna of the required length on a car and if we continue to use our ten or fifteen metre whip a considerable amount of negative reactance will appear. On forty metres this amounts to 1,200 ohms. It is therefore necessary to add enough positive reactance to cancel this out, in other words we must tune our whip to the required frequency. To do this a loading coil is added to the whip, and tuned until the inductance is just enough to cancel out the negative reactance.

An important point is the placement of this inductance as it will effect the

radiation resistance of the antenna to a great extent. With the loading coil at the base of the antenna, the radiation resistance will be approximately 4 ohms. With the coil in the centre, this is raised to about 10 ohms, and as a higher radiation resistance will give higher efficiency, the centre position is to be preferred. Top loading will give even higher efficiency, but this may be mechanically difficult to achieve.

See Figs. 1 and 2 for the current distribution on a bottom and centre loaded whip antenna. As the centre loaded antenna has more current flowing in it, it follows that this will have a higher field strength than the one with bottom loading.

The feeding of whip antennae will be covered in the following paragraphs.

CONSTRUCTION DETAILS

Now for details of an 8-foot centre loaded antenna for use on the 40 metre band. It is designed to have very low loss. The centre coil former is constructed from a piece of tubular polystyrene 1½ inches in diameter and about 4 inches long. Firstly, drill the ends as shown in Fig. 3. Sizes have been omitted as the diameter of disposal whips seems to vary quite an appreciable amount.


Next tap in the holding screws. This is best done by drilling a hole slightly under the size of the screw to be used. Then force the screw in, heating it every so often with a soldering iron.

When this is done, the thread for the winding can be cut in. This job must be done on a lathe of course, and it is best to have the other holes drilled at the same time, to ensure that they are all straight.

The coil is wound with 18 gauge tinned copper wire. About 52 turns at 18 turns per inch will be needed, the exact size must be determined by experiment, with the following procedure.

Fix the whip in place on the car and connect to transmitter through a length of 50 ohm co-ax cable. If the length of cable needed exceeds about six feet, it will be advisable to connect two pieces in parallel. Make sure that the co-ax is properly earthed at both ends. Couple the co-ax to the final tank coil of the transmitter with a two-turn link. Turn the transmitter on and note the loading. This must be done with the boot lid of the car down as far as possible.

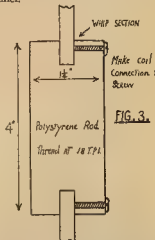Next, connect a length of stiff wire around the whip at the top of the coil and tapping it down a turn at a time until maximum loading is reached. Remove the number of turns shorted out and the job is done. To weather-proof the coil, give it one coat of clear enamel.



For 80 metres the procedure is similar except that approximately twice the number of turns will be required on the coil. It would be possible to construct an antenna which would cover both 40 and 80 metres by arranging a tap on the coil for 40 metre operation.

RADIO TECHNICIAN WANTED

Universal and exclusive opportunity offered for territories of Victoria and Queensland to energetic Radio Technician (Ham for preference) by established progressive N.S.W. electronic manufacturer of two-way h.f. radio equipment custom built for small ships, bush fire, mobile, light aircraft, etc. Applicants must have ability to organise sales, install and service. Arrangement will be on exclusive agency basis, carry liberal commission on sales. Apply in confidence with details of experience and references to Box 1761, G.P.O., Sydney, N.S.W.



WATCH FOR 1956 KIT SETS



GLORAD ENGINEERING SERVICES

291a TOORONGA ROAD, MALVERN, S.E.6, VIC. Phone: BY 3774



Trail of wreckage left by the 1955 Maitland flood.

Aborigines were Wiser than the Whites

Aborigines were wiser than their white counterparts when it came to settlement in the Hunter River Valley district of New South Wales.

They kept to the surrounding hills — safe from the avalanche of water which they knew could bring sudden death and disaster.

Early in 1955, the worst flood in the history of the white man in Australia swept through the valley, causing privation and misery to thousands of people.

It also cut every form of communication. More than 10,000 subscribers' services and 400 trunk lines and telegraph channels were cut off

and it was estimated that the repair bill would total more than £500,000.

Safeguard for The Future. It was a costly lesson, but today science has found a way to reduce this sort of flood damage to a minimum. A new resin* which permanently seals telephone terminal boxes in a solid waterproof block is being used by the Postmaster General's Department on its services throughout Australia.

SHELL scientists derived this resin from mineral oil to give communications the most effective waterproofing agent yet developed.

*Epukote Resin



SHORT WAVE LISTENERS' SECTION*

Well boys, I'm warning you that you'll have to spark yourselves up, or be shown up. That's right, and by a YL, too. S.W.I. Lola Burton has only been listening on the Amateur bands for a few months, but has already picked up most of the lingo, and as evidenced by the list of reports, quite a few stations too. We welcome you to the S.W.I. Group, Lola.

Greetings are extended to another S.W.I. Alan Holmes, who read about our Group in some copies of "A.R." loaned to him by a friend. Alan tells of his disappointment at not receiving a good percentage of returns to his reports. Well, cheer up Alan, we have all been through the same trouble at some time or other.

It may be well worthwhile to make a few suggestions on sending reports to short wave stations. When forwarding reports, the following information is a MUST: The call sign or other identification sign of the station heard, if an Amateur station, the call of the station being worked, the frequency, at least approximate, on which the station was heard, date and time, preferably G.M.T. The readability, signal strength, and if a c.w. station, tone, should be given. It is always a help to send a short resume of the conversation heard, or if a broadcasting station, brief details of the received programme should be given. If there are any aspects about the transmission which appear peculiar, mention should be made of these together with as accurate a description of the effects as you can give. Most important of all, make your reports genuine. If a station is perfectly readable he need not necessarily be strength 9. I might also point out that a station, say in the United States, possibly may not appreciate a report from an Australian S.W.I. on a contact with an Australian Amateur. As is obvious, he will have already received a report from the station contacted at least days before your report can reach him.

It is usually the station whose signal strength is down who would like to know just where their signals are going. Most of the 89 signals

may therefore be disregarded as far as sending reports are concerned. Of course, if it's a rare one you hear, send him a report by all means. One more don't. Do not send a report to a local station who is working DX unless you consider that you can really make the report useful.

VICTORIAN S.W.I. GROUP

The January meeting of the Group was held in the rooms on Tuesday, 11th. The evening proved very interesting, the highlight of which was an attempt to operate equipment on 388 Mc under the direction of Ian Woodman. Ian is one of the L.A.O.C.F. holders who regularly attends our meetings. Unfortunately no communication was established with any station. Len Poynter did a very fine job organising the set-up, and appeared quite blown out at the finish. The meeting ended with everybody happy despite the lack of success, and a discussion on transmission lines would have provided quite good entertainment had not the time been running on. Another attempt may be made from the rooms in the near future.

For the benefit of any person interested, the S.W.I. Group meets on the last Tuesday in every month at the Institute Rooms, 181 Queen Street, Melbourne. Any person at all interested in radio is welcome to attend our meetings.

The Group would like to hear from any Amateur who would be willing to come to one of our meetings and give a lecture or short talk on some aspect of Amateur communication. If you do not feel at your ease attempting something of this nature, perhaps a visit of about five or six members to your shack could be arranged. If you can help us in any way, please contact the Secretary of the Group, John Wilson, 37 Raymond Street, Alphington, Vic., or ring Ian Hunt at FD 0861 Ext. 387 during the day.

We hope to hear more of the exploits of Groups in other States. Come on you boys in VK2, VK4, VK5, VK6 and VK7. Let us hear a lot more from you.

REPORTS OF AMATEUR BANDS

Ladies first, as always. YL S.W.I. Lola Burton reports hearing the following stations: 21 Mc.—WPKC, VIERG, LX181. 14 Mc.—HKS-FV, VVIBD, VSSUW, ODEY, HZITA, CERO,

VPIE! WBSB, WSEY, WAHK!, CEVSE, ETU-US, PYAYC, YVEDL, KP4WD, MPBBDW, LUG-D, WGLI, KASCI, ZSY, WBGIZ, GSCQK, WBRUC, WAKK, KASZ, YQAG, OHBZ, HP3PL, KADDB, KX0BU, KAILG, WGGUK, F08AB, YIZAM, WSTLZ, CNEMM VPIJH, LUS-DIE, KCHWD, XZ3SS, TIELA, DLARP, VETIB, GW4CP, GANF.

WIA-13025 made available a list of stations but did not indicate the bands on which these stations were active.

WIA 13015, Michael Ida, submits the following list of stations: 28 Mc. KH8BS, W6VAD, 14 Mc.—JAAV, GMCDL, V56CG, TGRAL, KASW, HZITA, V1238, ZMAAT, KP4WD, ODS-AS, VVSAG, KX0BU, VBI8C, ZSSJM, K166Q, V88ER, 4878R, KV48R, KH8BS has also received cards from CNEMM, EMSA and VSEVW.

WIA-13087 has managed to make his receiver perk long enough to receive the following 14 Mc.—KH8BU, K184-B, KASCI, V1238, W4MZX, KX6MK, ZP4H, ZSSNO, KZ5AD, W4DF, K3KAC, HP18H, VK1U, EATGW, V28-AC, ZMAAT, KX02B, KH8BS, K8BAH/P, CBWTS, GFW, GWBHN, KACN, JAAV, VU2-SS, ZSSJM, CT1PK, KZ3S, H80ET, PY2CK, KP4BD, ZK18B, V1WQN, VK80G, V80CH. Cards have been received from ZS15W and ZS19C.

Other cards being held for members of the S.W.I. Group are from PY68F, DL1JY, WPKC, WFLD and W6DI. Keep these reports coming in together with any other dope you may have on hand. More material is what we want. Station descriptions, reports, or hints and tricks you think someone else may be able to use, any of these details are welcome. Address your correspondence to John Wilson, whose address is given above, or to Ian J. Hunt, 181 Robert Street, Northcote.

CHANGE OF ADDRESS

W.I.A. members are requested to promptly notify any change of address to their Divisional Secretary, net direct to "Amateur Radio."

AN OPEN LETTER

Logically, the outstanding performance of TRIMAX PRODUCTS implies that they are not always the cheapest available, but there is that assurance of long-life and efficient service which is synonymous with Trimax quality.

In the long run, TRIMAX gives you the best value for your money . . . maintenance costs are cut . . . and performance is trouble-free and continuously efficient.

Let TRIMAX solve your transformer problems.



TRIMAX

PTY. LTD.

FOR TRANSFORMERS OF QUALITY

CNR. WILLIAMS ROAD & CHARLES STREET, NORTH COBURG, VIC.

FL 1701

TRIMAX FAMOUS PRODUCTS

include

- Power Transformers and Chokes up to the largest air-cooled sizes.
- All types of Audio and Modulation Transformers.
- Hi-Fidelity, astatically wound Audio Transformers.
- Audio Amplifiers and Equipment.
- Nickel-iron alloy Shields for Transformers, Cathode Ray Tubes, etc., for reducing pick-up from external fields.
- Standard and special steel Chassis and Cabinets.
- Relay Racks, Table and Floor Microphone Stands.
- Electrical Connectors.
- Voltage Regulating Transformers: capacity 50 VA., etc.

FIFTY-SIX MEGACYCLES AND ABOVE

V.h.f. DX has been excellent lately. On the 50 Mc. band openings have occurred VK4 and VK4 from VK3. On 10/11/56 the VK4 worked 2, 3, 4, and 7. On 12/11/56 ZL2DS broke through to VK3 for a short period. On 10/11/56 at 2010 hours E.S.T. VK1IJ of Macquarie Island reports hearing VK4GG and VK4HT at R5 and S8. On 22/11/56 VK4NG reports working JAI4HS at 1440 to 1447 hours E.S.T. The JA reported VK4NG at R5 S9 and he gave the JA R5 S8. VK4NG also heard JAI4EW.

VICTORIES

Athol SCP has built up a new converter using a 6BQ7A as a neutralized p.p. triode, with a 6X4 rectifier and grid-rectifier mixer, with a cathode follower in the output. The xtal is an 11.5 Mc. 6AG5 mixer is on its fundamental and the plate circuit is tuned to the fourth harmonic with a second 6AG5 trebling to 130 Mc. The AR89 is tuned from 8 to 10 Mc. It is working very well and Athol is happy with the results he has been obtaining.

The programme for the last V.h.f. meeting included two short lectures, the first by Bob 30J on "An interference unit of disposable 'Intangs,'" and the second by 6ZAA and 6HK, who gave a short talk on the v.h.f. activity in VK8. The result of the first v.h.f. field day for this season was announced, first place and 11 minutes of air time to George 30J, second Len R.N. and third Reg 3ZAD. Following the second field day on 13th Feb., which coincided with the National Field Day, it was decided to hold a further field day on 18th Mar. This day coincided with the V.h.f. Autumn Field Day, and details of rules were given at v.h.f. field days for this season, see copy of "A.R." for Jan., 1966, p. 16.

The v.h.f. meeting in April, to be held on Wednesday, 18th, will be the city-country get-together and will be held at the rooms, 191 Queen Street.

V.L. DX has been excellent lately. On 144 Mc. TFF and 7LZ have been worked by several of the VK3 gang. They are on most nights looking for VK3 contacts, calling on the hour and 10 minutes past the hour. The frequency is approx. 180 degrees. The VK3 country stations have been coming through into Melbourne at very good strengths and a couple of them have been heard as far away as Sydney was audible. They are SVY of Sals and 3ZAB of Traralgon. Stan 3ZAB had his first contact into Melbourne some weeks ago when he contacted 6XJ from the Gippsland area. There have been on from the Gippsland area are 8VL, JUS and JDJ of Leonagatha, and 8ZD of Warragul. George 8GM is still maintaining his log book and reports that he has been receiving remitting enthusiasm and has now placed a beam on the top of a 100 ft steel poppet tower on the site at Mt. Dunnington. He has been working 144 Mc. every night since he started on the hour and has got through on a number of occasions. On 144 Mc., look for SWH on Thursday and Friday nights. Sheds are kept open for 144 Mc. on Wednesdays and Thursdays listens for SWH from 2130 to 2140 hours.

During the holiday week-end Laurie 3ALY, with Bob 3QJ and Len 3LN, went portable on top of a hill at Portlinton. While tuning his rig, Laurie heard 3JY at Sale working 3ZD at Warragul and he used the standard low frequency technique of giving a short break when 3JY was transmitting and Len and Bob nearly fell out of the car with amusement when 3ZD gave a break acknowledging 3ALY's call. Then followed a 100 per cent three-way contact between Sale, Warragul and Portlinton.

If you're after a VKS contact on the 144 Mc. band, keep a check on approx. 144.1 Mc. for 3RS at Albany, who calls each evening at 8 p.m. with the beam towards Melbourne. The bearing of Albany from Melbourne is approx. 40 degrees.

8HK and 8ZAA operated mobile whilst on a holiday trip to Melbourne and were eagerly sought after by the VKs for contacts and contest numbers.

Stations with gear for the 56.40 Mc. band include 3XM, 3AHL, 3YJ, 3YS, 3CI, 3OF, 3VL and 3US. 3VL and 3US, who are located in Leongatha, operate on 56.50 Mc. and are looking for contacts after about 8 a.m. each evening.

The low ebb of the band that we saw all missed so much during the past few months. It is also very pleasing to hear the long absence of Jim Dale back on the band again. Even if he has to hound me to get him to go to do it. Herb JJO, President of the V.A.F. Gear, is making steady progress on the way to his own station. The new ZALY will have to curb his radio activity (nothing to do with transium) during the next year or two. He is planning to build on the crevasse. Maybe this will mean some of the other chaps, as well as Laurie and the way, there'll be more DX for others. I am sure that the missing piece of the standing is now missing from the 3 mx band. Jan SALE now has the a.c. connected and has been working on it with his hand gear operator—Phyl Moneux.

NORTH KOREANS

Last month was a very busy one for the w.h.f. boys in this State. We were very pleased to meet in person and entertain (we hope) Don SHK and Wally SZAA from Perth. Don had mobile gear for 144 Mc. and together with mobiles SGL, BEK and SBT, much fun was had by all, as they say.

From Mr. Lorty all the mobiles QSOed EBC on 144 Mc with signals ranging from 590 to 599 on phone. At Mr. Lorty it is no trouble to work Hughes with a 10 watt mobile tx and a cat radial aerial adjusted for a quarter wave on 144 Mc as a vertical radiator. Signs vary from S4-S5 at both ends. Many mobile to mobile tests have been carried out between Ken S5C and your scribe and in future issues I propose to give more details of the tx's and rx's which are in use. I hope that there may be of some help to any others who are perhaps interested in going mobile.

Reg SQR with renewed vigour has erected a 18 el phased array for 144 Mc. and is very pleased with the results so far. He has also constructed a xtal locked converter for 300 Mc. and with similar gear to be constructed by George SOB. they hope to "shatter" the existing Australian one mhz record; best of luck chaps!

There has been little activity in the country on 144 Mc except of course for the very reliable and consistent signal of 5BC in Renmark. I believe 5EN has been on only a couple of occasions and 3EY in Gawler has also been very quiet. The city boys however have been quite active and one can now call CQ even while mobile and generally succeed in having a contact. Neil 5ZAW, Phil 5ZAD and Ian 5ZAA have been on 1 max fairly consistently over the past month.

The DX season on 80 Mc. has been extremely poor as far as VKs is concerned. Col SRO Hugh 5BC and Reg 5QR have been active, but few contacts have been had, due mainly to a general lack of stations and not necessarily poor conditions.

Bob SPU has built a nice xtal converter for 288 Mc. and this, used in conjunction with a planned xtal tx to be built by SMT, should be instrumental in extending the 288 Mc. record distance of 106 miles.—SMT.

WESTERN AUSTRALIA

The February meeting of the V.h.f. Group heard an informative lecture from Don SZAV on his experiments with skeleton slits. Don came complete with models of the arrays and from the many questions asked it was very evident how interesting his talk had been. John SZAV was welcomed to the meeting and an apology was received from another new member, 6ZAJ, who is in National Service.

144 Me.: Event of the month has been the Dawn Patrol activity. Wally GWO in Albany has been heard consistently at 0915 hours Perth over the 346 mile path. His signal has been heard by both GZAY & GZAX. GZAX has also been heard in Albany but no reports have been exchanged to date. Ralph GZAD and Cecil GZAZ in Perth and Don GDW in Bruce have also heard Wally. Signals have been received from Wally at 0815 hours for a period of 14 days, but not always at a workable strength. Of interest is the fact that the signals at 0815 hours are consistently better than those at 0915 hours. It appears that you must realize your noise DX!

Another item of interest was the copying of Don GHK's mobile tx (10w to a halo) from outside Northam (50 miles) through hilly terrain. With a beam and higher power, what would signals from Northam be like?

Dardanup and SZAL in Bunbury. Checks between SZAH and EXI have been very successful with mod. osc. type gear.

Also promising well is the news that Frank SFB found much interest in v.h.f. in Geraldton. At least one person has taken the exam and likely to obtain a 2 call. Jim SJH is also interested. Ralph SZAD has been temporarily shifted to Forest on the Trans. line and hopes to have checks with Perth over the 400-mile path. Best wishes to you, Ralph!

The news of this country activity is very encouraging. It appears that with at least 30 watts and a good beam—say a stacked yagi or phased array—and a good converter—cascode or 836 type—distances up to 80-100 miles should be consistently good. For longer hauls, however, higher power would be desirable.

Again the offer of the V.h.t. Group is repeated. If you would like a demonstration of V.h.t. gear at your QTH or any help at all to get gear going, then contact your scribe—Wally Nowse, 53 Ellen Street, Fremantle (phone 41 1363), who will arrange for the resources of the Group to help you.—SZAA.

THE UNIVERSITY OF CHICAGO

January has seen a lot of activity on 144 Mc in Launceston. VK's stations have been worked by TGM, TIZ, TFF on eight days, the best opening being on the 22nd when TFF worked 18 VK's, TIZ managed 4 VK's, and TGM missed out entirely. This made TGM suspect his new five over five, but later openings make it seem as if H was just bad luck. Much has been learnt from these openings. Signals usually did not become much good until 1100 and then the band stayed open until at least 2400 hours.

Often the hardest part of working into VKK is getting someone to hear you. Some VKKs are can matter. TLE is all set for ulcers after hearing stations rag chewing for hours with strengths up to 80 and this with the VKKs beams side on. The openings apparently were due to mainly local inversions, no subsidence inversion being around.

The scoring system in the Ross Hull Contest does not take into account Interstate working on 144 Mc. as the Laurenceon gang can double their points for working a local three miles away, making 10 points for a first contact while VK9, 300 miles away, only rates 5 points.

With the increased activity beams seem to be the main subject. IGM has put up a new five over five and TBQ and TLZ are going to try a five over five also. TLZ is changing beams since finding that the feeder to his present 11-el. array gets hot every half wavelength. TP3 is working on beam theory for a beam to end all beams.—TPE.

D.X.C.C. LISTING

Listed below are the highest twelve members in each section. New members and those whose totals have been amended will also be shown.

PHONE

Call	Cer No.	Crit- ria	Call	Cer No.	Crit- ria
VK4PJ	21	382	VK4UD	1	152
VK3BZ	3	176	VK4NS	8	153
VK4HR	13	176	VK6KW	4	156
VK6RU	2	170	VK6LN	11	141
VK3ATN	26	165	VK6RW	23	141
VK3EE	18	152	VK3AWW	24	140

C.W.

Call	Cer.	Cnt.	Call	Cer.	Cnt.
	No.	ries		No.	ries
VK5HZ	8	323	VK5BY	45	181
VK3FH	19	310	VK3CX	38	180
VK4FJ	29	306	VK4EL	9	177
VK4HR	4	300	VK3CN	1	163
VK3KB	10	300	VK4RU	18	161
VK3ZO	3	183	VK3RX	23	156

Auswertung

20

OPEN					
Call	Cer. No.	Cnt-ries	Call	Cer. No.	Cnt-ries
VKSHZ	4	331	VKINS	18	181
VKACX	5	335	VKHG	3	181
VKAPJ	33	317	VK4EL	10	175
VK4HR	7	314	VK5KW	13	171
VK8SU	8	304	VK4DI	3	171
VK4JE	13	186	VK4DO	14	171

FEDERAL, QSL, and DIVISIONAL NOTES

FEDERAL

Fed. President: W. T. Mitchell, VK3DQ.
Fed. Secretary: D. D. Doyle, VK3DQ, Box 3611W, G.P.O., Melbourne.
QSL Bureau: R. E. Jones, VK3RJ, 33 Landale Street, Box Hill, Vic.
DZ AA: A. J. Weynton, VK3XU, 30 Park St., West Brunswick, N.10, Vic.

NEW SOUTH WALES

President: Jim Corbin, VK3YC.
Secretary: Harry Rickie, VK3ACH, Box 1734, G.P.O., Sydney.
Meeting Night: Fourth Friday of each month at Science House, Gloucester Street, Sydney.
Divisional Sub-Editor: Ted Whiting, VK3ACD, 16 Linden Street, Five Dock.
QSL Bureau: J. B. Corbin, VK3YC, Box 1734, G.P.O., Sydney (Inwards and Outwards).
Zone Correspondents: North Coast and Tablelands: Noe Hanson, VK3ASH, Ryan Ave. West Kempsey, Newcastle; Ron McD. Stuart, VK3AJS, 48 Dunbar St., Stockton, Cessnock and Laker, Harry Hawkins, VK3VL, 9 Confort Ave., Cessnock; Western: W. H. Bitt, VK3VH, "Cambridge", Forbes; E. East and Southern: Eric Fisher, VK3DZ, 3 Oxide St., Warragabri; South Western: B. Edge, VK3AJJ, Wallace St., Coolamon; St. George: Gene Coyle, VK3YK, 44 Carlton Cres., Kogarah; Eastern: Walther, Barry White, VK3AAB, 35 Flavelle St., Concord.

VICTORIA

President: G. Dennis, VK3VF.
Secretary: D. L. Robinson, VK3ALD.
Administrative Secretary: Mary May, C.O.R. House, 191 Queen St., Melbourne.

Meeting Night: First Wednesday of each month at Radio Society, Melbourne Technical College.

Divisional Sub-Editor: Phil Menzies, 235 Union Road, Ascot Vale.

QSL Bureau: Inwards and Outwards—W.I.A., 191 Queen St., Melbourne, C.I., Vic.

Zone Correspondents: Central Western: W. J. Kinsella, VK3AKW, Magdala, Lubbeck; South Western: W. Wilson, 48 Cranley St., Warrambool; and W. Zimmer, VK3AW, 79 Stone St., Newtown, North Eastern: A. D. Buchanan, VK3JD, "Broodmoor", Wahing, Far North Western: M. Felle, VK3QJ, 181 Glenview Ave., Mildura; Eastern: K. V. Scott, VK3SS, Johnston St., Maffra; Northern Western: C. Case, Cumming Ave., Birchlip.

QUEENSLAND

President: Frank Bond, VK3KM.

Secretary: W. J. Ratner, VK3PR, Box 683J, G.P.O., Brisbane.

Meeting Night: Fourth Friday in each month at the Royal Geographical Society Rooms, Ann Street, City.

Divisional Sub-Editors: F. B. Bond, VK3KM, and W. J. Ratner, VK3PR.

QSL Bureau: Inwards, Files, VK3JF, Wren St., Buranda, Outwards—Miss Clair O'Brien, 83 Jardine St., Stafford.

SOUTH AUSTRALIA

President: G. M. Bowen, VK3XU.

Secretary: B. W. Austin, VK3CA, Box 124K, G.P.O., Adelaide. Telephone: UX 2611.

Meeting Night: Second Tuesday of each month at 17 Wymouth St., Adelaide.

Divisional Sub-Editor: J. M. Coultier, VK3JD, 69 Conmura Ave., Ackland Gardens.

QSL Bureau: Geo Luxton, VK3RX, 37 Belair Rd., North Mitcham, S.A. (Inwards and Outwards).

WESTERN AUSTRALIA

President: F. A. T. Tredrea, VK3FT.
Secretary: J. Mead, VK3GJ, Box N1029, G.P.O., Perth, W.A.

Meeting Place: Perth Technical College Annex, Mounts Bay Road, Perth.

Meeting Night: Third Tuesday of the month.

Divisional Sub-Editor: R. H. Atkinson, VK3WZ, P.O. Box 127, Geraldton.

QSL Bureau: Jim Jones, VK3RU, Box F319, G.P.O., Perth, W.A. (Inwards and Outwards).

TASMANIA

President: F. J. Evans, VK3FI.
Secretary: W. G. Tall, Box 311B, G.P.O., Hobart.

Meeting Night: First Wednesday of each month at the W.I.A. Club Room, 148 Liverpool St., Hobart.

Divisional Sub-Editor: V. F. Dore, VK3JD, 29 Brent St., Glenorchy.

QSL Bureau: K. A. Johnston, VK3RX, 34 Tower Rd., Newnham.

Zone Correspondents: Northern: M. A. Chaplin, P.O. Box 56, Threlklyn Rd., Lumsden, North Western: S. P. Hatfield, VK3UW, 30 Mark St., Burnie, Tas.

PAPUA-NEW GUINEA

President: F. M. Nolan, VK3WN.

Secretary: D. F. Lloyd, VK3QO, C/o. O.T.C. Receiving Station, Port Moresby.

Divisional Sub-Editors: Holland, VK3EW, C/o. P.O. Box 76, Rabaul.

QSL Bureau: D. H. Beadel, VK3DS, C/o. P.O. Box 107, Port Moresby.

FEDERAL

INTERNATIONAL GEOGRAPHICAL YEAR

1957-58

Federal Executive has been happy to receive from Professor H. C. Webster, of the Queensland University, a letter in which it is suggested that the International Geographical Year should be an important part of the scientific investigations of the International Geophysical Year 1957-58.

Quoting from his letter, Professor Webster says: "The phenomena of the aurora which is so especially examined in the 'aurora polaris'. As you know, the aurora australis is sometimes seen at E. Tasmania and the southern parts of continental Australia, and is regularly seen in the Australian antarctic dependencies.

"Dr. Gerson, of the U.S.A., has pointed out to me that Radio Amateurs operating in the 8-30 Mc. band can assist in the investigation of aurora by reporting evidence of freak reception on this frequency, particularly when the great circle joining the transmitter and receiver goes well south. Such freak transmissions can arise from reflections of the radio waves from the auroral discharge itself and thus add to our knowledge of the phenomena of the aurora.

The Professor goes on to say that he is most anxious to find out if any of our members would be willing and able to co-operate in such investigations. Federal Executive will reply to the Professor stating the matter will be put before members and they will supply him with the names of those interested.

In the past, Amateurs in Australia have had but little opportunity to be included in scientific investigations of such a high order. This therefore constitutes a challenge to the efforts and enthusiasm of members generally, be they v.l.f. or h.f. operators. It is a challenge offered by Professor Webster (who, incidentally, is Convener of the I.G.Y.) should be seized upon by all. This is the time when we must take our place along with other Amateurs in the Southern Hemisphere in some worthy scientific research.

In order that organisation shall be on a Divisional basis, members are requested to send their names into their Divisional Headquarters at the earliest possible moment so that Professor Webster may be informed and plans prepared. This is a real opportunity.

DX CONDITIONS AND SUNSPOTS

With the rapid improvement in DX conditions the following information, kindly made available by the Amateur Administration, is of great interest and suggests well for the next few years.

The forthcoming Sunspot Maximum is likely to be Unusually Early and High

"As is well known, conditions of astronomical observations throughout the world keep a constant watch on the sun in order to determine the daily occurrence of the number of sunspots. The latter and its frequency of occurrence influence on the ionisation of the ionosphere, which in turn determines the propagation conditions of radio waves. It is also well known that the approximate length of a cycle is about 11 years.

"The Secretariat of the C.C.I.R. constantly follows, with great interest, the results of these astronomical observations, and the predictions made by several radio organisations of the expected value of the sun's activity in the months to come.

"We wish to draw the attention of all users of radio waves to the unexpected very rapid rise of the observed 'provisional sunspot number' which took place during November, 1955. Indeed this rapid rise far superseded all predictions known to us.

"There is an empirical rule, deduced from many earlier observations, stating that a forthcoming sunspot maximum will be the higher the faster the sunspot numbers increase during the beginning of the build-up of a new cycle. The last minimum occurred during the middle of 1954, and at present we are in the build-up phase of a new cycle. The build-up is now occurring at an exceptionally rapid rate so that, in all probability, the next sunspot maximum will be of outstanding intensity. Professor M. Waldmeier, Director of the Zurich Astronomical Observatory, the well known expert in this field, expects the highest 'monthly sunspot number' to be about 150, or even larger. Moreover, he expects the coming sunspot maximum to surpass all the previous maxima so far observed, and he predicts that this maximum will be reached as early as the middle of 1957.

"The above extrapolations prove to be accurate we may expect the change to higher frequencies for long distance radio communications to be necessary for a number of months. It has been generally thought it is for the reason that we herewith draw the attention of all concerned to this unexpected phenomenon."

Prof. Dr. Balch, Director, C.C.I.R.

T.V. TEST TRANSMISSIONS

Those Amateurs who are interested in preparing and testing t.v. receivers will be interested to know that a signal is available in Adelaide and Melbourne, and is portable but are of such type as to be suitable for receiver checking.

The Adelaide transmission is on Channel 2, 189-191 Mc. while in Melbourne it is Channel 10, 209-215 Mc.

FEDERAL QSL BUREAU

RAY JONES, VK3RI, MANAGER

Divisional QSL Managers and others are requested to note the changed address of the U.C.A.R. QSL Bureau which now is Q36AO, G. Pagny, Rue 2006 Elisabethville, Belgium.

Clovet, FASDA, writing under date of Dec. 26, states he has just received from FASRW a bundle of VK3 cards dating back to 1949/51. He has hastened to reply to them all.

The Association Radio Ecuadorian, whose QSL Bureau is Box 229, Quito, Ecuador, has supplied an up to date list of all addresses.

Amateurs, any QTH is available on application to the Federal Bureau.

Alan Ferriman, VK3PO, ex-VK1J, Munich 37, Germany, advises that they will handle cards for DL1, DL4, DL5 and DL6 in addition to DL1, 1, 6, 7, 9 and DL7, 1, 2, 3 and DL call signs.

Alan Ferriman, VK3PO, ex-VK1J, advises under date of 1st Feb. that he has been exceptionally busy since returning from the far south. Alan has moved six times in the two years since his return, got married and spent a lot of time in travel between Adelaide and Woomera. He is firm in his intention to send out all cards and hopes to achieve this in the near future.

John "Paddy" Bloughton, on Maljoro Island in the Marshall group and is the former KCZBZ of Yap Island in the Western Carolines. Paddy is now on 14 Mc. phone with a Viking tr and a long wire antenna and will QSL all contacts for both call signs.

David Johns, who operated VK3ID at Macquarie Island in 1954, has sent out 300 cards through the various Bureaus. Anyone who has missed out, David at 28 Waterworks Road, Hobart, Tasmania.

Terry Knodlock, VK3AD, ex-ZLAF, who operates from the P.O. Box 125 station on Cala Bay, Fiji, has a nice card portraying local scenery. Card is available for all contacts.

John "Paddy" Bloughton, on Maljoro Island, Italian Somaliland, is currently active on 14 Mc. c.w. around 1530x and has a strong signal, but is monopolised by the powerful D stations.

FEDERAL AWARDS

NEW COUNTRIES

The following additions have been made to the DXCC Countries List 1/54 (XWB), Cambodia (1978) and Viet Nam (1953) and credits were given to stations for confirmation of contacts made on or after 20th July, 1955.

As of 19th July, 1955, credits will no longer be made in listing shown as French Indo China (FIC). Credits for French Indo China contacts must show the contact date prior to 20th July, 1955.

W.A.V.K.C.A. AWARDS

Certificates have been issued to 0N4AU, ZL4GX, VE2AY, 3B0D, G2AG, WQ3HH, and ZL4FZ. A total of 26 certificates have been issued to 31/7/55.

G. Weynton, VK1XU, Awards Manager

VICTORIA

The first general meeting for the year was very poorly attended, in fact the worst general meeting in post-war years. Possibly the reason for this was the cancellation of the scheduled lecture. This was a great pity as Fred, 3VS, went to an enormous amount of trouble to arrange what turned out to be a most enjoyable programme. It took the form of short lectures pertaining to field days and with the National Field Day imminent, the choice of subject was most appropriate. Fred 3VS started off the lectures by giving a resume of the rules and conditions of field day in general. This was followed by Harry 3OU who gave an illustrated description of a simple modulator for car radio modulation of the Type 8 Mark 2. This in turn was followed by Hans 3AHR who spoke on a battery operated v.f.o. and also on the use of a portable transmitter. His lecture with blackboard diagrams. Then Len 3LN gave his experiences and advice on what to do and particularly what not to do on a field day. Len's experiences are very wide and very varied as he has participated in every field day in the post war period. This was then followed by David 3VW who gave a description of an all band v.f.o. controlled portable piece of equipment. At the conclusion of these lectures, Bill 3W, who has recently returned from a trip abroad, gave a very amusing and interesting talk on his experiences in the U.K. with special emphasis on his visit to the R.S.G.B. Headquarters and to the Radio Show conducted by the R.S.G.B. Bill, with his very dry humour, mentioned that he had no language difficulties whatsoever while travelling through the U.K. He gave us lots of laughs and those present enjoyed his wit and also hearing of his experiences.

The following were welcomed as new members to the Institute. Full members—Messrs. R. Scott (3OB), W. Carlyle (3IP), B. Gillies (3AGG), G. Macfarlane (3ATM), W. Michie (3ZCM), and N. Kay; Associates—Messrs. J. McEwen, R. Hughes, Norman, J. Macdon, and J. Macdon. R. Hargrave, J. Shaw, R. Owen, R. Davis, N. Henderson, J. Murray, J. Dunn, J. Pittman, R. McEwen, and A. McKean.

The next general meeting of the Institute, to be held on Wednesday, 19th March, will be the postponed lecture on t.v. which will be given by Mr. Kempson, a member of the Melbourne Technical College staff, and will be based on the new t.v. operator's commercial license.

80 METRE TRANSMITTER HUNT

A good crowd attended the last 80 metre tx hunt, which was held in perfect sunshine. The tx was hidden by Len 3LN at Cranbottle Cove, which is in a very inaccessible position from the Melbourne direction. It is on the coast at the back of Point Cook R.A.A.F. station. Here 3LN found the uplink set-up where a

farmer had laid out nearly a mile and a half of nicely insulated electric fences around his property. Len bridged them all together and took a fine wire some 400 feet over a road to the tx hidden in box trees bushes.

Laurie 3ALY was first on the location but took nearly an hour to find the tx by unbridging the various sections. He then went down the position of the hidden tx. He was followed by Roy 3ALY and Reg 3ZAD. The harmonics made most of the beach and enjoyed a swim and a picnic. Len 3LN gathered on the beach to finish off a pleasant afternoon. The next 30 m tx hunt will be held on Sunday 28th March, when the tx will be hidden by Len 3LV.

BI-MONTHLY SCRAMBLE, DEC. RESULTS

The second Bi-Monthly Victorian Scramble was held on 8th December, 1955. Although a total of 36 stations participated, only eight logs were received! The winner was 2ALY with 19 points, all earned on 144 Mc.

Section C: 3ALY 19, 3ADW 15, 3AER 15, 3ZAG 13, 3ADL 11, 3W1 8, 3OJ 7, 3ZD 5.

Checking: 3HE and 3AHH.

The results of the February Scramble, held on 8th February, 1956, will be announced in the next issue. Transmitting Amateurs resident in the State of Victoria and Short Wave Listeners resident in the Commonwealth of Australia are reminded that the next Scramble will take place on 2nd April, 1956 (Easter Monday). How about making it a complete success? Remember, there is more than one section, and the top scorer in each section is entitled to a very attractive certificate! OK, send in your log by the 30th April, '56! Rules of this Scramble can be found on page 13 of "A.R." September, 1955. Send your log to the Divisional Contest Manager, W.L.A., Vlc. Div., 191 Queen Street, Melbourne, C.I. Good luck! 3AHH.

ROBIN MEMBERS STORY

The zone generally sounds to be very busy lately, quite a lot of activity on the various bands although there is more to report. One of our zone members, G. Munday, has now commenced a new job with Len 3DX in radio, so looks as though he will be guided on the air in time with a little 3DX tuition. 3EO has been mobile in VK3 using one of 3AGD's 3R whip. 3EQ and Bill Wines spent a few hours with the Type 8 Mark 2 before 3EQ went to VK3. 3AHR has been heard again, keep it up Kev. Brian 3UT is on now and again. Harry 3DZ is on the short wave, also a new beam approx. 100 ft high, so should go places.

Bill Wines is starting to get busy for the Convention which will be held in Warrnambool on the week-end, 17th and 18th March, so hope to see quite a lot of chaps turn up as it will be a good show. Also anyone who requires accommodation must let Bill Wines know before 3rd March as it is hard to get bookings otherwise we will be able to make arrangements for caravans if required. Hope to see the XYLs come along.

Chris 3AKU has sent the following: Ron 3CK has been away on holidays. Gordon 3Eon has been busy with his new rig, while Mart 3AKU has been busy on 30 m with his AT5/AR8 combination. 3AGV seems to have a good score in the 30 m contest, he has also been on 28 Mc. Chris 3AKU has been inactive as he is busy shifting to new QTH and getting the AT5 going. During January 3AC called on 3AGV and 3AGV was on 30 m with a QSO with Col 3FO and Col couldn't believe his ears when 3AC clipped in, he thought he was hearing things. 3AGV woke up that David was in 3AGV's shack. Well chaps hope to see a lot of you in our city for the Convention.

NORTH EASTERN ZONE

Stan 3AGD seems to be in quite an impressive stranglehold for a new collector. George 3GD received quite an issue of cards from his 21 Mc. folded dipoles. Tom 3ETX thought to have been in on it too. Col 3WQ passed out the cards as one of his last jobs in this zone. As 3ALY is doing back on the 30 m, Bruce 3AGG and Brian 3ASZ are on 30 m. Johnny 3ACK is returning to Radio when business permits. Murray 3WZ is on 30 m with a Wangerite & white back. There is nothing of Alex's (3AT) activities. Peter 3APF is in with Alan 3UJ and Syd 3CI on the 3 m. Keith 3IC is not back on the 30 m. According to Des 3CO, Doug 3IL said that the temperature at Macquarie Island was up around 43 degrees during the day. That was at the beginning of the year though.

Unfortunately the Euro VLS frequency that Associate Jim Hargrave works on is a bit too low for standard Amateur equipment. Des 3BP was away on holidays on last advice. Henry 3BP is working hard on his VLS skeds with assistance from Howard 3TV Jack 3AGC and his XYL, now at a new address, are receiving congratulations on the arrival of a son on 4th Dec. Jim 3IK has a new Collins 75A type 3 rx now. Bruce 3QC has loaned Bill 3AJW a tx. 3AMZ is now in Wangaratta. 3IZ was up that way on a trip back to Maryborough, and Doug 3EO was up here with a Type 3 portable. Ron 3AQG was to get some help from Associate Ken Mercer putting in his antenna. 3QL has been heard opening in Bright. Secretary Earle Sootes is on shift work now. Ray 3PI is not ready to go on the air yet. Ken 3KJ reports DX on 30 m is quiet.

80 METRE ZONE

A welcome voice on the 80 m hook-up was Bill 3WE who has not been heard for some time. Very pleased to hear the old sig again. Ron 3PR comes on regularly; has grid leak bias in now and a clamper tube; talking of

Low Drift Crystals

FOR AMATEUR BANDS

ACCURACY 0.02% OF
STATED FREQUENCY

3.5 Mc. and 7 Mc.

Unmounted £2 0 0

Mounted £2 10 0

12.5 and 14 Mc. Fundamental
Crystals, "Low Drift,"
Mounted only, £5.

THESE PRICES DO NOT
INCLUDE SALES TAX.

Spot Frequency Crystals
Prices on Application.

Regrinds £1 0 0

MAXWELL HOWDEN

15 CLAREMONT CRES.,
CANTERBURY, E7,
VICTORIA

VICTORIAN DIV., W.L.A. SOUTH WESTERN ZONE

CONVENTION

will be held at

WARRNAMBOOL

on

SAT. & SUN., MAR. 17 & 18

For accommodation, apply—

N. J. WINES, 48 Crawley Street,
Warrnambool, Vic.



A & R OUTPUT TRANSFORMERS

★ TYPE 921 (921-8: 2 or 8 ohms; 921-15: 3.7 or 15 ohms):

For VALVES:
807, KT66,
etc.
Suitable Conversion
"WILLIAMSON" & U.L.
See "Audio Engineering" of
June, 1962.

30 WATTS: 20-30,000 c.p.s.
Primary: 4,500 ohms.
SCREEN TAPS: 10% of Plate Z.
F.R.: Plus or minus 1 db 10-50,000
c.p.s.
Leakage Inductance:
1/2P/1/2F: 15 mH. maximum.
Prim/Sec: 30 mH. maximum.

★ TYPE 931 (931-8: 2 or 8 ohms; 931-15: 3.7 or 15 ohms):

For VALVES:
614, EL37,
KT66, etc.
See "Radio and Hobbies" of
February, 1962, 17 watts
U.L. Amplifier

30 WATTS: 20-30,000 c.p.s.
Primary: 4,500 ohms.
SCREEN TAPS: 10% of Plate Z.
F.R.: Plus or minus 1 db 10-50,000
c.p.s.
Leakage Inductance:
1/2P/1/2F: 15 mH. Maximum.
Prim/Sec: 15 mH. maximum.

★ Ultra Linear Output Type—

Type 916—12 watts.
Prim.: 4,500 ohms p.p. (with
screen taps).
Sec.: 216-5, 5 or 8 ohms;
916-15 3.7 or 15 ohms.
Type 918—15 watts.
Prim.: 4,500 ohms p.p.
Sec.: 2, 8, 12.5 15 ohms.
Response: 10-50,000 c.p.s.
Valves: 6V6, 6BW6, KT66,
EL84, etc.
10% Screen Taps.

★ For Mullard "5-10" Amplifier

Type 2545—12 watts.
Prim.: 4,500 ohms c.d.
Sec.: As below.
Response: 10-50,000 c.p.s.
Type 2506—3 watts.
For 2 or 8 ohms Secondary.
Type 2506—15 watts.
For 3.7 or 15 ohms Secondary.

PERFORMANCE
DEPENDABILITY
APPEARANCE
QUALITY

MANUFACTURED BY—
A & R ELECTRONIC EQUIPMENT CO. PTY. LTD.
378 ST. KILDA ROAD, MELBOURNE, VIC.
Details from these **EXCLUSIVE A & R DISTRIBUTORS!**
QUEENSLAND: A. E. Harrold, 128 Charlotte St., Bris.
TASMANIA: Homocraft Pty. Ltd., 220 Elizabeth St., Hobart
WEST. AUST.: A. J. Wyle Pty. Ltd., 1411 Hay St., Perth.

SYDNEY — N.S.W.: United Radio Distributors P/L, 175 Phillip St.
SOUTH AUST.: Gerard & Goodman Ltd., 196 Rundle St., Adelaide.
MELBOURNE & VIC.: J. H. Magrath & Co. Pty. Ltd., Homocraft Pty. Ltd., Model Spares Ltd., Radio Parts Pty. Ltd., Warburton Frankl Ltd.

STOP PRESS

AVAILABLE MARCH!

Radio Amateur Handbook

1956 EDITION

Published by the Amateur Radio Relay League

Price **44/3**, and **2/-** postage

ORDER NOW

This is a Radio Book no Amateur or Professional can do without

From— McGILL'S AUTHORISED NEWSAGENCY

183-185 ELIZABETH STREET, MELBOURNE, C.1, VICTORIA
(The Post Office is opposite) Phones: MY 1475-76-77

Page 23

chance of good outside contacts due to very bad electrical interference, the display was impressive and did a lot of good to improve the facilities on Amateur Radio as hobby. The excellence of the display was due to the time which Mr. Jim Parris was able to give during the days of preparation. The display tried and true contacts with SWL, the Institute is grateful. The Organizers were very thrilled with the co-operation that they received from the Council and the staff again that we assist them during March, 1956.

Tape Recordings and Technical Data. In order to help contacts and to help again, Council has continued its policy of supplying tape recordings of technical lectures to centres where a recorder is available. In order to supplement those already made, a new series is to be made of technical topics which are useful members.

Q.100. **SWL.** Mr. C. J. O'Brien (50N) found that he would have to relinquish the office of operator early last year and since that time the station has been operated by the President. Sometimes Council have wondered if the Sunday morning broadcasts to our country members are fulfilling a real need, but I can assure you that these broadcasts are looked forward to in the shacks of our distant friends.

March 1956. Following an appeal for technical articles earlier this year, the sub-editor has received four already with a promise of two more. The hardware section is always in demand by country and city members. More are still needed to pass our previous record. I am sure that there is plenty of material. In order to help contacts and to help again, Council has continued its policy of supplying tape recordings of technical lectures to centres where a recorder is available. In order to supplement those already made, a new series is to be made of technical topics which are useful members.

General. Following an appeal for technical articles earlier this year, the sub-editor has received four already with a promise of two more. The hardware section is always in demand by country and city members. More are still needed to pass our previous record. I am sure that there is plenty of material. In order to help contacts and to help again, Council has continued its policy of supplying tape recordings of technical lectures to centres where a recorder is available. In order to supplement those already made, a new series is to be made of technical topics which are useful members.

General. Following an appeal for technical articles earlier this year, the sub-editor has received four already with a promise of two more. The hardware section is always in demand by country and city members. More are still needed to pass our previous record. I am sure that there is plenty of material. In order to help contacts and to help again, Council has continued its policy of supplying tape recordings of technical lectures to centres where a recorder is available. In order to supplement those already made, a new series is to be made of technical topics which are useful members.

General. Following an appeal for technical articles earlier this year, the sub-editor has received four already with a promise of two more. The hardware section is always in demand by country and city members. More are still needed to pass our previous record. I am sure that there is plenty of material. In order to help contacts and to help again, Council has continued its policy of supplying tape recordings of technical lectures to centres where a recorder is available. In order to supplement those already made, a new series is to be made of technical topics which are useful members.

General. Following an appeal for technical articles earlier this year, the sub-editor has received four already with a promise of two more. The hardware section is always in demand by country and city members. More are still needed to pass our previous record. I am sure that there is plenty of material. In order to help contacts and to help again, Council has continued its policy of supplying tape recordings of technical lectures to centres where a recorder is available. In order to supplement those already made, a new series is to be made of technical topics which are useful members.

General. Following an appeal for technical articles earlier this year, the sub-editor has received four already with a promise of two more. The hardware section is always in demand by country and city members. More are still needed to pass our previous record. I am sure that there is plenty of material. In order to help contacts and to help again, Council has continued its policy of supplying tape recordings of technical lectures to centres where a recorder is available. In order to supplement those already made, a new series is to be made of technical topics which are useful members.

General. Following an appeal for technical articles earlier this year, the sub-editor has received four already with a promise of two more. The hardware section is always in demand by country and city members. More are still needed to pass our previous record. I am sure that there is plenty of material. In order to help contacts and to help again, Council has continued its policy of supplying tape recordings of technical lectures to centres where a recorder is available. In order to supplement those already made, a new series is to be made of technical topics which are useful members.

General. Following an appeal for technical articles earlier this year, the sub-editor has received four already with a promise of two more. The hardware section is always in demand by country and city members. More are still needed to pass our previous record. I am sure that there is plenty of material. In order to help contacts and to help again, Council has continued its policy of supplying tape recordings of technical lectures to centres where a recorder is available. In order to supplement those already made, a new series is to be made of technical topics which are useful members.

General. Following an appeal for technical articles earlier this year, the sub-editor has received four already with a promise of two more. The hardware section is always in demand by country and city members. More are still needed to pass our previous record. I am sure that there is plenty of material. In order to help contacts and to help again, Council has continued its policy of supplying tape recordings of technical lectures to centres where a recorder is available. In order to supplement those already made, a new series is to be made of technical topics which are useful members.

General. Following an appeal for technical articles earlier this year, the sub-editor has received four already with a promise of two more. The hardware section is always in demand by country and city members. More are still needed to pass our previous record. I am sure that there is plenty of material. In order to help contacts and to help again, Council has continued its policy of supplying tape recordings of technical lectures to centres where a recorder is available. In order to supplement those already made, a new series is to be made of technical topics which are useful members.

General. Following an appeal for technical articles earlier this year, the sub-editor has received four already with a promise of two more. The hardware section is always in demand by country and city members. More are still needed to pass our previous record. I am sure that there is plenty of material. In order to help contacts and to help again, Council has continued its policy of supplying tape recordings of technical lectures to centres where a recorder is available. In order to supplement those already made, a new series is to be made of technical topics which are useful members.

General. Following an appeal for technical articles earlier this year, the sub-editor has received four already with a promise of two more. The hardware section is always in demand by country and city members. More are still needed to pass our previous record. I am sure that there is plenty of material. In order to help contacts and to help again, Council has continued its policy of supplying tape recordings of technical lectures to centres where a recorder is available. In order to supplement those already made, a new series is to be made of technical topics which are useful members.

General. Following an appeal for technical articles earlier this year, the sub-editor has received four already with a promise of two more. The hardware section is always in demand by country and city members. More are still needed to pass our previous record. I am sure that there is plenty of material. In order to help contacts and to help again, Council has continued its policy of supplying tape recordings of technical lectures to centres where a recorder is available. In order to supplement those already made, a new series is to be made of technical topics which are useful members.

and GRU. An important item of agenda was the election of the Federal Councillor. BGM had resigned the position, as he would be unable to attend the Federal Convention proposed to be held this year. The election resulted in the appointment of Ron SKW as Councillor. A vote of thanks was also recorded, in appreciation of his long term of service.

FOR moved that certain action be taken to review the present position of limited licences under the General Code and has been proposed that a sub-committee be formed to make enquiries and submit recommendations to the General Code Committee. The members of the sub-committee. We believe Tom and Rollo are at work and making good progress.

GKX moved that the evening, with a lecture on t.v.l. and the t.v.l. proofing of transmitters, illustrating his lecture with a piece of American equipment. A hand-switched 500 to 15 to 144 Mc.

Tom also promised a film evening in the near future: films of his recent tour of England and the Continent. This should be very interesting.

Don SKK and Wally GZAA recently returned from their tour of the VK5-VK3 shacks. We believe they had an interesting trip, also the VKK call on 144 Mc. caused some near heart failures in certain VK3 shacks!

A had a mail call on 7 Mc. Mr. GEE, Bob, late 3ASH. Glad to meet you Bob and hope you make many friends in VK3.

W indicated that he had received a very good letter. UA3, UC, UI, VU and JA coming through at good strength. Hope you are making out well.

An opportunity, rare in Amateur Radio, will shortly take place. VK6 will be providing radio communications for the Marignac Car Club which will be held in the near future.

Not yet to hand, but tentative arrangements re equipment and men are being made. This should be held in the near future.

Radio in this State. For those who wish to listen, the frequencies are 3.34 and 8.71 Mc. The date is week-end ending March 11-12E.

TASMANIA

The general meeting for February was held on the 1st of the month, with President 7FJ in the chair and Secretary Bill Tait in attendance. A representative gathering of members was present, the general business section of the meeting, several suggestions in connection with the Olympic Games and the World Radio Week.

Federal Executive approval has been given to a suggestion emanating from Mark TMM that a relay be arranged conveyed to the Greek Amateur Radio Olympian in Greece to the Australian Olympic Games Committee. The relay to be handled this end via Amateurs operating on the medium wave band.

Other suggestions discussed, and under consideration are (1) That this year's VK-ZL Contest be held to coincide with the opening of the Olympic Games, and (2) That world wide greetings be relayed to the Games Committee from Amateurs in all parts of the world.

A committee was also appointed to investigate the equipment and operator angles of the Emergency Network, the immediate aim being co-operation with the Sea and Rescue Section of the Bush Walking Club.

At the conclusion of business, Mr. Tas. Fehlbauer delivered a lecture on the subject of "The World of Radio" and his effort was greatly appreciated by the members.

Athol TAJ is convalescing and hopes to be active again soon. Better stoke up the old rig Athol and let's hear from you. Doc TLL has come on line again to England and back for about a year, so doubtless he will entice some new equipment home with him when he returns.

Lon TLL is in the middle of a rebuilding campaign, but is taking time off now and then to think about possible sites for a new relay station. The VKA anticipate running a Geloop now not for the portable 7 Mc. tx. and at the time of writing are seeking a generator power supply for the job. It is hoped that a new relay station will come to light with a brand new tx. complete with all mod. cons. and t.v.l. proof. This plus relay station will make a formidable force to be reckoned with in the next R.D. Contest. That reminds me also that Peter TPA has attended the Federal Convention and returned. Is he Peter? Reach for that send switch and let's see what happens.

TCH has been holidaying in the Sandford area, but I am not sure whether Snowy took any equipment with him, or whether it is a holiday in the complete sense of the word. Len TLL has been camping, but is now back in harness again.

Doubtless all members are by now aware that the Divisional General Convention will take place at Brunette Park on 10th March.

Organisation is in the capable hands of Reg TWN and colleagues, and everything seems set for a really good function. Harry TBR and I have been asked to be in a position to handle any mobile work that any of the visitors contemplate on the journey to Brunette, so if any of you mobile gentry are interested, you had better get in touch with Harry, pronto, if you have not already done so. Greeting cards are extended by GZAA, who will be living down this way for some time. Unfortunately, I do not know the names at the time of writing, but we won't let that detract from the welcome that VK3 will soon be changed to one with a VK7 prefix. Tom TAJ has been subjecting himself to the rigours of a small Araldite casting, he has bought a nice new sky-blue Zephyr as compensation. Who is going to keep the dust off the wheels of this car, which will be such a counter attraction. Nicky TRY is operating crystal control, but a new v.f.o. is under way and should be in operation in the near future.

PAPUA-NEW GUINEA

As a sub-editor has not yet been appointed for this year, GRM was asked to supply notes. The Divisional meeting was held on 7th March, and at year's end I am pleased to say that nearly all Amateurs in the Territory are active. The weather has been very good, with conditions prevailing up here, whereby most residents go south for leave every two years, there are usually several of the fraternity away enjoying the fruits of a holiday. At times it becomes quite a problem to make up a quorum of councillors to deal with Divisional matters. From the weekend of March 10th, the small Division speaks well for the interest and activity of its members and we all look forward to continued success and growth in the ensuing year.

On leave at this moment is our first President HVT, who needs no introduction here or in VK3. He will be back in the Territory in about three months. Also others taking the same treatment are SAG from Wewak and BDT of Port Moresby.

The purchase recently of a large rig for the use of SWI for local, hook-ups on Sunday morning during the holidays should go a long way to welding the Division even closer, as the topography in the Territory is not exactly conducive to 7 Mc. GSCs. Rabaul has always been a tough one to contact, and with quite a few members located there on the rim of a submerged volcano, we look forward to the putting some added r.f. in their direction.

We welcome two new members in SAS at Wewak and SAG at Port Moresby. Both have been active in the hook-ups since joining up. Also leaving for us for keeps is the oldest member, namely Ron SRC after 35 years in New Guinea—some 20 years in the Division! Ron has always been active over the years and now looking forward to a well earned rest around the VKI gap. Incidentally, he has held a call since 1910 and has seen it all from aloft jars and cable antennae, right up to the modern day. I have no doubt will shortly be conversant with t.v.l.

As your scribe is holding the fort until a new sub-editor for local news is duly elected for the year, would welcome any expression of interest for inclusion in these notes.—GRM.

1/- per line, minimum 3/-

Advertisements under this heading will only be accepted from Institute Members who desire to dispose of surplus property which is their personal property. Copy must be received by 10th of the month, and remittance must accompany advertisement. Payment is made on the basis of an average of six words a line. Dealers' advertisements not accepted in this column.

FOR SALE: R.A.F. Type W86 Absorption Wavemeter, bandswitched to 15 Mc., £2/10/- Wanted: 1 inch Cathode Ray Tube. Lloyd, Tullamore, Humphries Rd, Frankston, Vic.

WANTED: H.R.O. Receiver. Slutskin, 8 Lynedoch Avenue, East St. Kilda, Vic.

WANTED: 35Z Transmitter, any condition. Ward, 23 Dawson Avenue, Elwood, Vic. (XM 1000).

WESTERN AUSTRALIA

The January meeting of the Division was held in the Tech. School Annex. The names of the Divisional representatives on the Advisory Committee were released for the first time as follows: GAW, BOR, GZAA, GKK, ENF

Homecrafts

AMATEURS' BARGAIN CENTRE

BUILD YOUR OWN SHORT WAVE RECEIVER

using the
KINGSLEY KBS2 COIL UNIT
WITH R.F. STAGE

FEATURING BAND SPREADING
on the 31 Metre, 25 Metre, and 19 Metre Bands
also covers the Broadcast Band.

PRICE £9/12/0 Plus Tax

DIAL GLASS to suit, 10/8 Plus Tax

Also the

KINGSLEY KBS1 COIL UNIT

as above, but less R.F. Stage

PRICE £6/16/0 Plus Tax

OTHER KINGSLEY COIL UNITS IN STOCK

Type KU3 Dual Wave Bracket 66/8 Plus Tax

Type KU4 Dual Wave Bracket with R.F. 116/- Plus Tax

FOR THE HI-FI FAN

Coils to suit the Wide Band Tuner 64/- Plus Tax

COIL FORMERS

R.C.S. Polystyrene Six-Pin Base—

1½ inch diameter 3/3 Plus Tax

1½ inch diameter 3/7½ Plus Tax

Q Plus 5/16 inch diameter, complete with screwed Iron Core 3/4 Plus Tax

Q Plus Coil Dope 2/4 Plus Tax

SET BUILDING SIMPLIFIED

Q PLUS PRE-FAB. TUNING UNITS

Only require connection to power supply and L.F. channel. No alignment necessary.

TYPE QW5

features Band Spread

on the 31 Metre, 25 Metre, and 19 Metre Bands
in addition to Broadcast coverage.

PRICE £8/2/9 Plus Tax

TYPE QWR5

as above, but with R.F. Stage

PRICE £14/14/0 Plus Tax

DIAL GLASS to suit, 7/10 Plus Tax

Q PLUS SHORT WAVE COILS

13 to 42 Metres, or
16 to 50 Metres 5/- Plus Tax

50 to 150 Metres 6/8 Plus Tax

BARGAINS

Marquis Rib Type Coil Formers 1/11 each

1H6G Valves 2/- each

30K, 47K, 100K 2 Watt Resistors 5/- dozen

Phone Jacks 2/6 each

Carbon Microphone Inserts 5/- each

0-20 Volt Meters, 5 Ma. movement 11/9 each

200 Ohm Heavy Duty Rheostats 9/11 each

8" Ext. Speaker Boxes (walnut or white) 19/11 ea.

290 LONSDALE STREET, MELBOURNE

FB 3711



Attention is drawn to the

BRITISH EDDYSTONE 770 VHF and UHF COMMUNICATIONS RECEIVERS

Superbly engineered and of advanced design, the two models offered possess excellent electrical characteristics and are robustly constructed for service in any climate. The "770R" has continuous AM/FM coverage from 19 Mc. to 165 Mc.; the "770U" from 150 Mc. to 500 Mc. Both incorporate six-position turret tuning assemblies of unique design and giving high reliability. Self-contained when operated from a.c. mains and with provision for use of external power supplies.

★
*Specially
suited for
Monitoring
Field Tests,
Laboratory,
etc.*
★

Fully descriptive literature with illustrations and performance curves is available on request from the Australian Factory Representative:—



R. H. CUNNINGHAM PTY. LTD.
118 WATLETREE ROAD, ARMADALE, S.E.3, VIC.
and 184 VICTORIA ROAD, DRUMMOYNE, N.S.W.